

Electricity and Magnetism

Lecture 13 - Physics 121


Electromagnetic Oscillations in LC & LCR Circuits,

Y&F Chapter 30, Sec. 5 - 6

Alternating Current Circuits, Y&F Chapter 31, Sec. 1 - 2


- **Summary: RC and LC circuits**
- **Mechanical Harmonic Oscillator**
- **LC Circuit Oscillations**
- **Damped Oscillations in an LCR Circuit**
- **AC Circuits, Phasors, Forced Oscillations**
- **Phase Relations for Current and Voltage in Simple Resistive, Capacitive, Inductive Circuits.**
- **Summary**

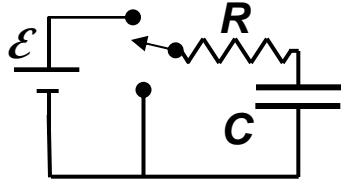Recap: LC and RC circuits with constant EMF - - Time dependent effects



$$V_C(t) = \frac{Q(t)}{C}$$

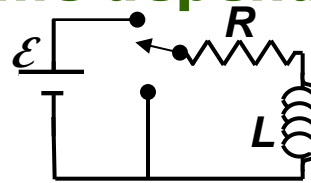$\tau_C \equiv RC \equiv$ capacitive time constant



$$\mathcal{E}_L(t) = -L \frac{di}{dt}$$

$\tau_L \equiv L/R \equiv$ inductive time constant

Growth Phase

$$Q(t) = Q_{\text{inf}}(1 - e^{-t/RC}) \quad Q_{\text{inf}} \equiv C\mathcal{E}$$


$$i(t) = i_{\text{inf}}(1 - e^{-t/\tau_L}) \quad i_{\text{inf}} \equiv \frac{\mathcal{E}}{R}$$

Decay Phase

$$Q(t) = Q_0 e^{-t/RC} \quad Q_0 \equiv C\mathcal{E}$$

$$i(t) = i_0 e^{-t/\tau_L} \quad i_0 \equiv \frac{\mathcal{E}}{R}$$

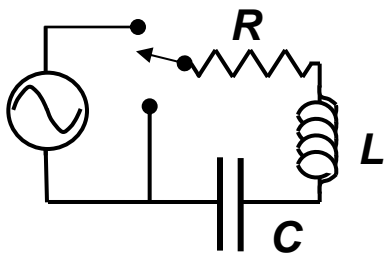Now LCR in same circuit, time varying EMF → New effects



- Generalized Resistances: Reactances, Impedance

$$R \quad X_C \equiv 1/(\omega C) \quad X_L \equiv \omega L \quad [\text{Ohms}]$$


$$Z \equiv \left[R^2 + (X_L - X_C)^2 \right]^{1/2}$$

- New behavior: Resonant Oscillation in LC Circuit

$$\omega_{\text{res}} = (LC)^{-1/2}$$

- New behavior: Damped Oscillation in LCR Circuit

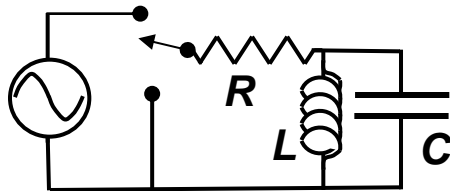- External AC can drive circuit, frequency $\omega_D = 2\pi f$




Recall: Resonant mechanical oscillations

Definition of an oscillating system:

- Periodic, repetitive behavior
- System state (t) = state(t + T) = ...= state(t + NT)
- T = period = time to complete one complete cycle
- State can mean: position and velocity, electric and magnetic fields,...

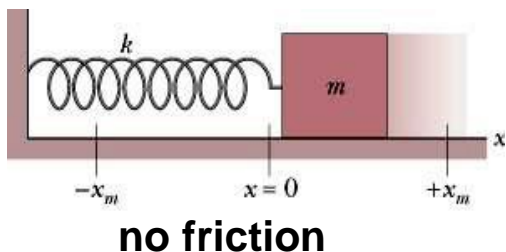Mechanical example: Spring oscillator (simple harmonic motion)



Hooke's Law restoring force : $F = -kx = ma$ **OR**

$$E_{\text{mech}} = \text{constant} = K_{\text{block}} + U_{\text{sp}} = \frac{1}{2}mv^2 + \frac{1}{2}kx^2$$

$$\frac{dE_{\text{mech}}}{dt} = 0 = m \frac{d^2x}{dt^2} \frac{dx}{dt} + kx \frac{dx}{dt} \quad v \equiv \frac{dx}{dt} \neq 0$$

Systems that oscillate obey equations like this...

$$\frac{d^2x}{dt^2} = -\omega_0^2 x \quad \omega_0 \equiv \sqrt{k/m}$$

With solutions like this...

$$x(t) = x_0 \cos(\omega_0 t + \phi)$$

What oscillates for a spring in SHM? position & velocity, spring force, Energy oscillates between 100% kinetic and 100% potential: $K_{\text{max}} = U_{\text{max}}$

Substitutions can convert mechanical to LC equations:

$$x \rightarrow Q \quad v \rightarrow i \quad m \rightarrow L \quad k \rightarrow 1/C \quad \omega_0^2 = k/m \rightarrow \omega_0^2 = 1/LC$$

$$U_{\text{el}} = \frac{1}{2}kx^2 \rightarrow U_C = \frac{1}{2} \frac{Q^2}{C}$$


$$K_{\text{block}} = \frac{1}{2}mv^2 \rightarrow U_L = \frac{1}{2}Li^2$$

Electrical Oscillations in an LC circuit, zero resistance

Charge capacitor fully to $Q_0 = C\mathcal{E}$ then switch to "b"

Kirchoff loop equation: $V_C - \mathcal{E}_L = 0$

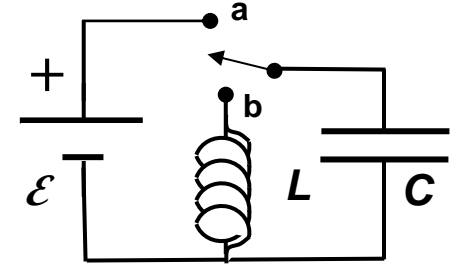Substitute: $V_C = \frac{Q}{C}$ and $\mathcal{E}_L = -L \frac{di}{dt} = -L \frac{d^2Q}{dt^2}$



$$\frac{d^2Q(t)}{dt^2} = -\frac{1}{LC}Q(t) \quad \text{An oscillator equation where } \sqrt{1/LC} \equiv \omega_0$$

solution: $Q(t) = Q_0 \cos(\omega_0 t + \phi) \quad Q_0 \equiv C\mathcal{E}$

$$i(t) = \frac{dQ(t)}{dt} = i_0 \sin(\omega_0 t + \phi) \quad i_0 \equiv \omega_0 Q_0$$

What oscillates? Charge, current, B & E fields, U_B , U_E

Peaks of current and charge are out of phase by 90°

$$\omega_0^2 = \frac{1}{\tau_C \tau_L}$$


where $\tau_C = RC$, $\tau_L = L/R$

Show: Total potential energy is constant $U_{\text{tot}} = U_E(t) + U_B(t)$

$$U_E = \frac{Q^2(t)}{2C} = \frac{Q_0^2}{2C} \cos^2(\omega_0 t + \phi) \quad U_B = \frac{Li^2(t)}{2} = \frac{Li_0^2}{2} \sin^2(\omega_0 t + \phi)$$

Peak Values Are Equal $U_{B_0} \equiv \frac{Li_0^2}{2} = \frac{L\omega_0^2 Q_0^2}{2} = \frac{LQ_0^2}{2} \frac{1}{LC} = \frac{Q_0^2}{2C} \equiv U_{E_0}$

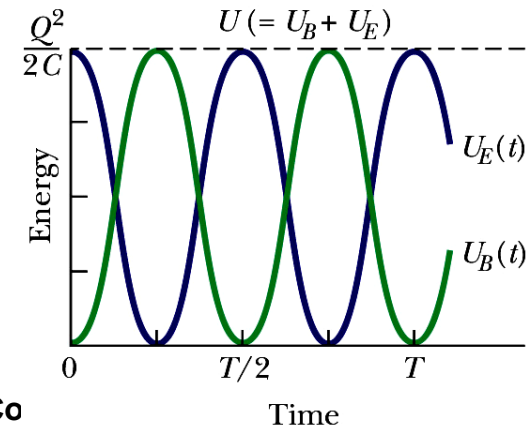$\Rightarrow U_{E_0} = U_{B_0} \Rightarrow U_{\text{tot}}$ is constant



Co

Time

Details: use energy conservation to deduce oscillations

- **The total energy:** $U = U_B + U_E = \frac{1}{2} Li(t)^2 + \frac{Q(t)^2}{2C}$
- **It is constant so:** $\frac{dU}{dt} = 0 = Li \frac{di}{dt} + \frac{Q}{C} \frac{dQ}{dt}$
- **The definitions** $i \equiv \frac{dQ}{dt}$ **and** $\frac{di}{dt} = \frac{d^2Q}{dt^2}$ **imply that:** $\frac{dQ}{dt} \left(L \frac{d^2Q}{dt^2} + \frac{Q}{C} \right) = 0$
- **Either** $\frac{dQ}{dt} = 0$ **(no current ever flows) or:** $\frac{d^2Q}{dt^2} + \frac{Q}{LC} = 0$ **oscillator equation**
- **Oscillator solution:** $Q = Q_0 \cos(\omega_0 t + \phi)$
- **To evaluate ω_0 :** plug the first and second derivatives of the solution into the differential equation.


$$\begin{aligned} \frac{dQ}{dt} &= -Q_0 \omega_0 \sin(\omega_0 t + \phi) \\ \frac{d^2Q}{dt^2} &= -Q_0 \omega_0^2 \cos(\omega_0 t + \phi) \end{aligned} \quad \Rightarrow \quad \frac{d^2Q}{dt^2} + \frac{Q}{LC} = Q_0 \cos(\omega_0 t + \phi) \left[-\omega_0^2 + \frac{1}{LC} \right] = 0$$

- **The resonant oscillation frequency ω_0 is:** $\omega_0 = \frac{1}{\sqrt{LC}}$ ight R. Janow – Fall 2013


Oscillations Forever?

13 – 1: What do you think will happen to the oscillations in a true LC circuit (versus a real circuit) over a long time?

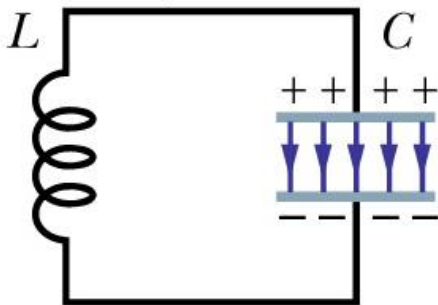
- A.They will stop after one complete cycle.**
- B.They will continue forever.**
- C.They will continue for awhile, and then suddenly stop.**
- D.They will continue for awhile, but eventually die away.**
- E.There is not enough information to tell what will happen.**



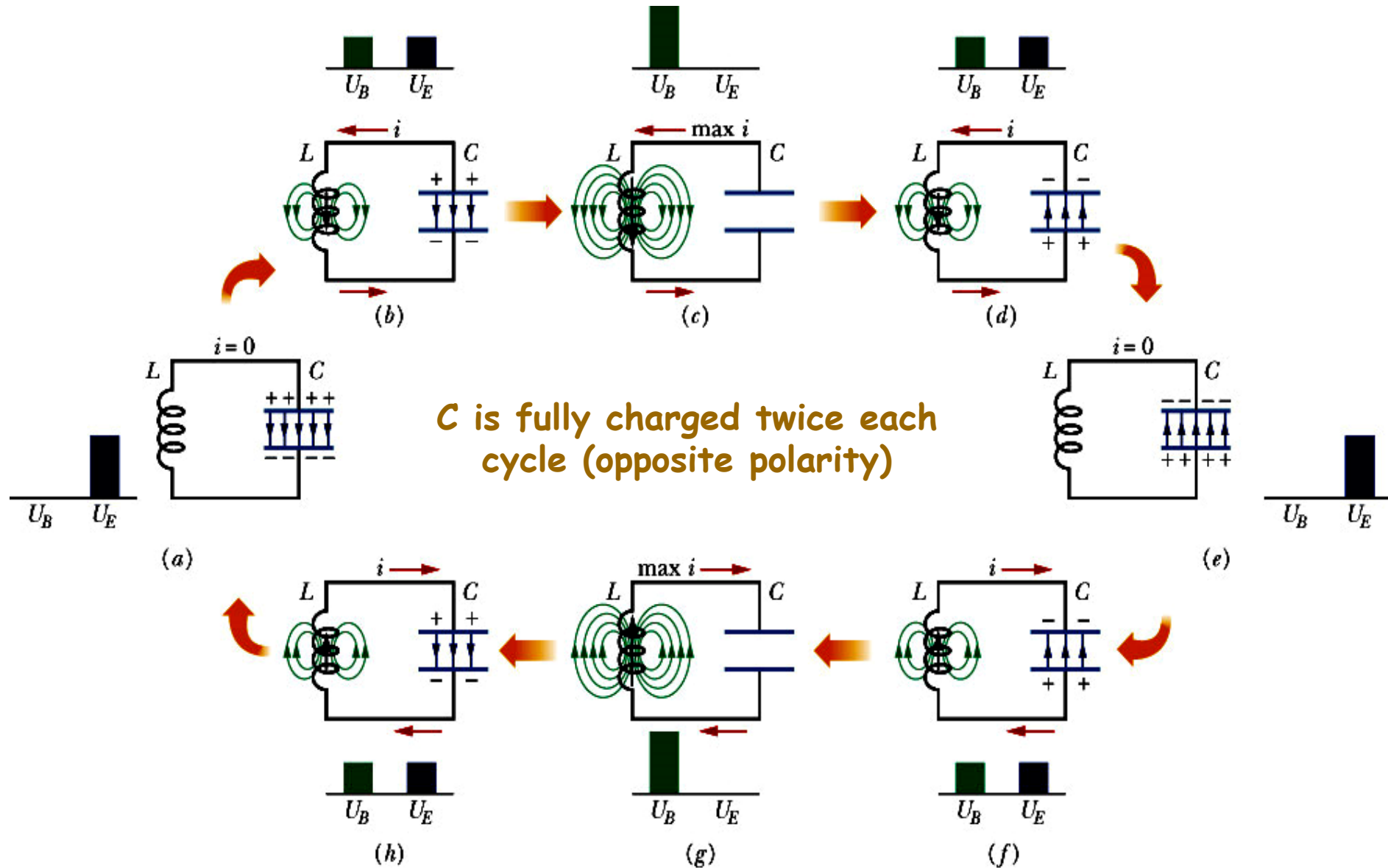Potential Energy alternates between all electrostatic and all magnetic – two reversals per period τ



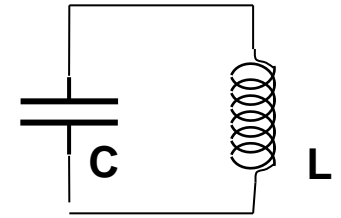Example: A 4 μF capacitor is charged to $\mathcal{E} = 5.0 \text{ V}$, and then discharged through a 0.3 Henry inductance in an LC circuit



Use preceding solutions with $\phi = 0$

a) Find the oscillation period and frequency $f = \omega / 2\pi$

$$\omega_0 = \frac{1}{\sqrt{LC}} = \frac{1}{\sqrt{(0.3)(4 \times 10^{-6})}}$$

$$= 913 \text{ rad/s}$$



$$f = \omega_0 / 2\pi = 145 \text{ Hz}$$

$$T = \text{Period} = \frac{1}{f} = \frac{2\pi}{\omega_0} = 6.9 \text{ ms}$$

b) Find the maximum (peak) current (differentiate $Q(t)$)

$$Q(t) = Q_0 \cos(\omega_0 t)$$

$$Q_0 = C\mathcal{E}$$



$$i(t) = \frac{dQ}{dt} = Q_0 \frac{d}{dt} \cos(\omega_0 t) = -Q_0 \omega_0 \sin_0(\omega_0 t)$$

$$i_{\max} = Q_0 \omega_0 = C\mathcal{E} \omega_0 = 4 \times 10^{-6} \times 5 \times 913 = 18 \text{ mA}$$

c) When does the first current maximum occur? When $|\sin(\omega_0 t)| = 1$

Maxima of $Q(t)$: All energy is in E field
 Maxima of $i(t)$: All energy is in B field
 Current maxima at $T/4, 3T/4, \dots (2n+1)T/4$



First One:
 $T = \frac{1}{f} = 6.9 \text{ ms} \Rightarrow T/4 = 1.7 \text{ ms}$
Others at:
 3.4 ms increments

Example

a) Find the voltage across the capacitor in the circuit as a function of time.

$$L = 30 \text{ mH}, \quad C = 100 \text{ } \mu\text{F}$$

The capacitor is charged to $Q_0 = 0.001 \text{ Coul.}$ at time $t = 0$.

The resonant frequency is:


$$\omega_0 = \frac{1}{\sqrt{LC}} = \frac{1}{\sqrt{(3 \times 10^{-2} \text{ H})(10^{-4} \text{ F})}} = 577.4 \text{ rad/s}$$

The voltage across the capacitor has the same time dependence as the charge:

$$V_C(t) = \frac{Q(t)}{C} = \frac{Q_0 \cos(\omega_0 t + \phi)}{C}$$

At time $t = 0$, $Q = Q_0$, so choose phase angle $\phi = 0$.
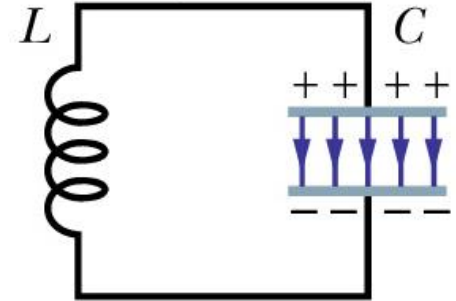
$$V_C(t) = \frac{10^{-3} \text{ C}}{10^{-4} \text{ F}} \cos(577t) = 10 \cos(577t) \text{ volts}$$



b) What is the expression for the current in the circuit? The current is:

$$i = \frac{dQ}{dt} = -Q_0 \omega_0 \sin(\omega_0 t) = -(10^{-3} \text{ C})(577 \text{ rad/s}) \sin(577t) = -0.577 \sin(577t) \text{ amps}$$


c) How long until the capacitor charge is reversed? That happens every $\frac{1}{2}$ period, given by:

$$\frac{T}{2} = \frac{\pi}{\omega_0} = 5.44 \text{ ms}$$

Which Current is Greatest?

13 – 2: The expressions below could be used to represent the charge on a capacitor in an LC circuit. Which one has the greatest maximum **current** magnitude?

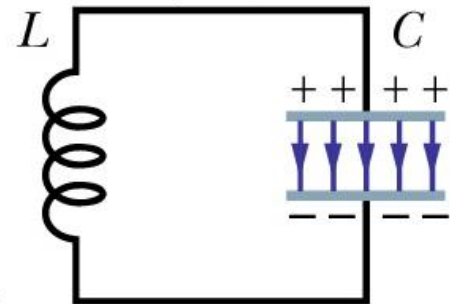- A. $Q(t) = 2 \sin(5t)$
- B. $Q(t) = 2 \cos(4t)$
- C. $Q(t) = 2 \cos(4t + \pi/2)$
- D. $Q(t) = 2 \sin(2t)$
- E. $Q(t) = 4 \cos(2t)$




$$Q(t) = Q_0 \cos(\omega_0 t + \phi) \qquad i = \frac{dQ(t)}{dt}$$




Time needed to discharge the capacitor in LC circuit

13 – 3: The three LC circuits below have identical inductors and capacitors. Order the circuits according to their oscillation frequency in ascending order.

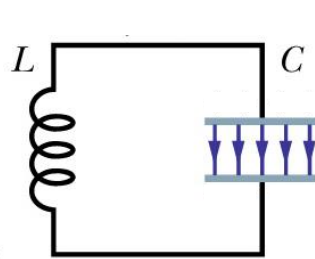
- A. I, II, III.
- B. II, I, III.
- C. III, I, II.
- D. III, II, I.
- E. II, III, I.



I.

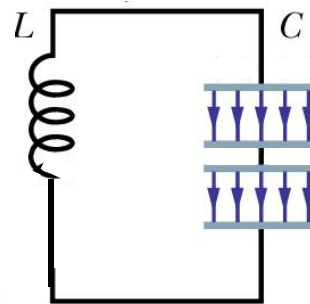

II.

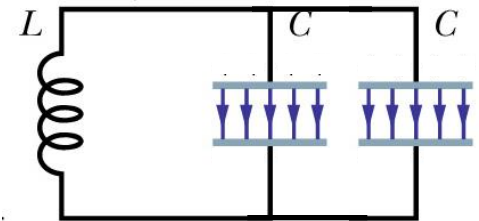

III.



$$\omega_0 \equiv \sqrt{1/LC} = \frac{2\pi}{T}$$


$$C_{\text{para}} \equiv \sum C_i$$

$$1/C_{\text{ser}} \equiv \sum 1/C_i$$

LCR circuits: Add series resistance

Circuits still oscillate but oscillation is *damped*

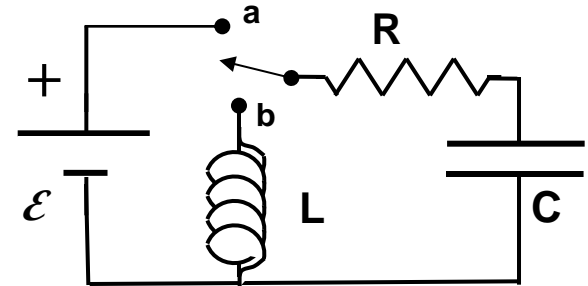Charge capacitor fully to $Q_0 = C\mathcal{E}$ then switch to "b"
 Stored energy decays with time due to resistance



$$U_{\text{tot}} = U_E(t) + U_B(t) = \frac{Q^2(t)}{2C} + \frac{Li^2(t)}{2}$$

Resistance dissipates stored energy. The power is:

$$\frac{dU_{\text{tot}}}{dt} = -i^2(t)R$$

Oscillator equation results, but with damping (decay) term

$$\frac{d^2Q(t)}{dt^2} + \frac{R}{L} \frac{dQ}{dt} + \omega_0^2 Q(t) = 0 \quad \omega_0 \equiv \sqrt{1/LC}$$


Solution is cosine with exponential decay (weak or under-damped case)

$$Q(t) = Q_0 e^{-Rt/2L} \cos(\omega' t + \phi) \quad Q_0 \equiv C\mathcal{E}$$

Shifted resonant frequency ω' can be real or imaginary


$$\omega' \equiv \left[\omega_0^2 - (R/2L)^2 \right]^{1/2}$$

Underdamped:

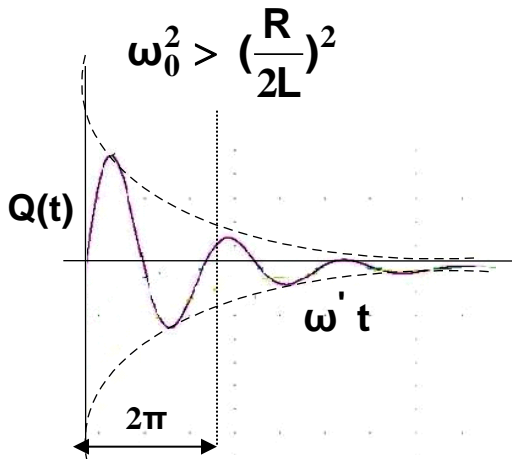


Critically damped

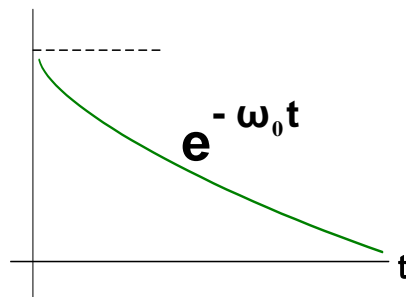$\omega' = 0 \quad \omega_0^2 = (R/2L)^2$



Overdamped

ω' is imaginary $\omega_0^2 < (R/2L)^2$

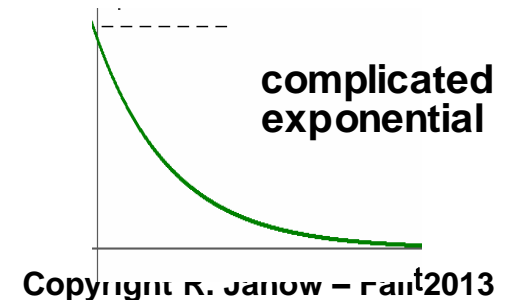

Resonant frequency with damping

13 – 4: How does the resonant frequency ω_0 for an ideal LC circuit (no resistance) compare with ω' for an under-damped circuit whose resistance cannot be ignored?

- A. The resonant frequency for the non-ideal, damped circuit is *higher* than for the ideal one ($\omega' > \omega_0$).
- B. The resonant frequency for the damped circuit is *lower* than for the ideal one ($\omega' < \omega_0$).
- C. The resistance in the circuit does not affect the resonant frequency—they are the same ($\omega' = \omega_0$).
- D. The damped circuit has an *imaginary* value of ω' .


$$\omega' \equiv \left[\omega_0^2 - (R/2L)^2 \right]^{1/2}$$



Alternating Current (AC) - EMF

- AC is easier to transmit than DC
- AC transmission voltage can be changed by using a transformer.
- Commercial electric power (home or office) is AC, not DC.
- The U.S., the AC frequency is 60 Hz. Most other countries use 50 Hz.

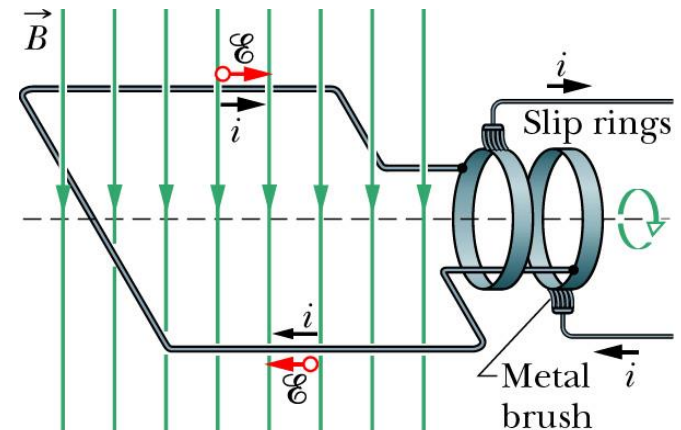- **Sketch: a crude AC generator.**
- EMF appears in a rotating a coil of wire in a magnetic field (Faraday's Law)
- Slip rings and brushes allow the EMF to be taken off the coil without twisting the wires.
- Generators convert mechanical energy to electrical energy. Power to rotate the coil can come from a water or steam turbine, windmill, or turbojet engine.



Represent outputs as sinusoidal functions:

$$\varepsilon_{\text{ind}}(t) = \varepsilon_m \sin \omega_d t$$
$$i = i_0 \sin(\omega_d t - \phi)$$

External AC EMF driving a circuit


External, sinusoidal, instantaneous EMF applied to load:

$$\mathcal{E}(t) = \mathcal{E}_{\max} \sin(\omega_D t) \quad \mathcal{E}_{\max} \equiv \text{amplitude}$$

The potential across the load $V_{\text{load}}(t) = \mathcal{E}(t)$

$\omega_D =$ the driving frequency

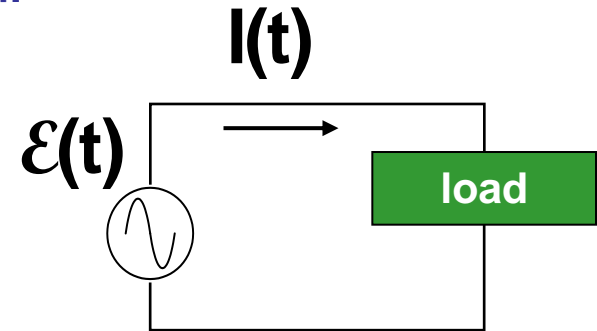$\omega_D \neq$ resonant frequency ω_0 , in general




Current in load flows with same frequency ω_D ...but may be retarded or advanced (relative to \mathcal{E}) by “phase angle” Φ (due to inertia L and stiffness $1/C$)
Current has the same amplitude and phase everywhere in a branch

$$I(t) = I_{\max} \sin(\omega_D t - \Phi)$$

Example:

Series LCR Circuit

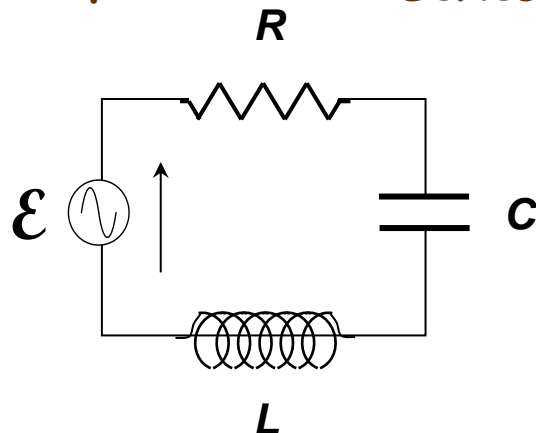

Everything oscillates at driving frequency ω_D

At “resonance”: $\omega_D = \omega_0 = \sqrt{1/LC}$

Φ is zero at resonance - circuit acts purely resistively.

Otherwise Φ is + or - (current leads or lags applied EMF)

Instantaneous, peak, average, and RMS quantities for AC circuits

$$\mathcal{E}(t) = \mathcal{E}_{\max} \sin(\omega_D t) \quad i(t) = i_{\max} \sin(\omega_D t - \Phi)$$

Instantaneous voltages and currents:

- depend on time through argument: ωt
- periodic, repetitive, oscillatory
- possibly advanced or retarded relative to each other by phase angles
- represented by rotating “phasors” - see below

Peak voltage and current amplitudes are just the coefficients out front

$$\mathcal{E}_{\max} \quad i_{\max}$$

Simple time averages of periodic quantities are zero (and useless).

- Example: Integrate over a whole number of periods - one τ is enough ($\omega t = 2\pi$)

$$\int_0^\tau \sin(\omega t - \Phi) dt = 0 \quad \text{Integrand is odd} \quad \Rightarrow \quad \begin{aligned} \mathcal{E}_{\text{av}} &\equiv \frac{1}{\tau} \int_0^\tau \mathcal{E}(t) dt = \mathcal{E}_{\max} \frac{1}{\tau} \int_0^\tau \sin(\omega_D t) dt = 0 \\ i_{\text{av}} &\equiv \frac{1}{\tau} \int_0^\tau i(t) dt = i_{\max} \frac{1}{\tau} \int_0^\tau \sin(\omega_D t - \Phi) dt = 0 \end{aligned}$$


“RMS” averages are used the way instantaneous quantities were in DC circuits

- “RMS” means “root, mean, squared”.

$$\frac{1}{\tau} \int_0^\tau \sin^2(\omega t - \Phi) dt = 1/2 \quad \text{Integrand is even} \quad \Rightarrow \quad \begin{aligned} \mathcal{E}_{\text{rms}} &\equiv \left[\langle \mathcal{E}^2 \rangle_{\text{av}} \right]^{1/2} = \left[\frac{1}{\tau} \int_0^\tau \mathcal{E}^2(t) dt \right]^{1/2} = \frac{\mathcal{E}_{\max}}{\sqrt{2}} \\ i_{\text{rms}} &\equiv \left[\langle i^2(t) \rangle_{\text{av}} \right]^{1/2} = \left[\frac{1}{\tau} \int_0^\tau i^2(t) dt \right]^{1/2} = \frac{i_{\max}}{\sqrt{2}} \end{aligned} \quad 013$$




Phasor Picture:

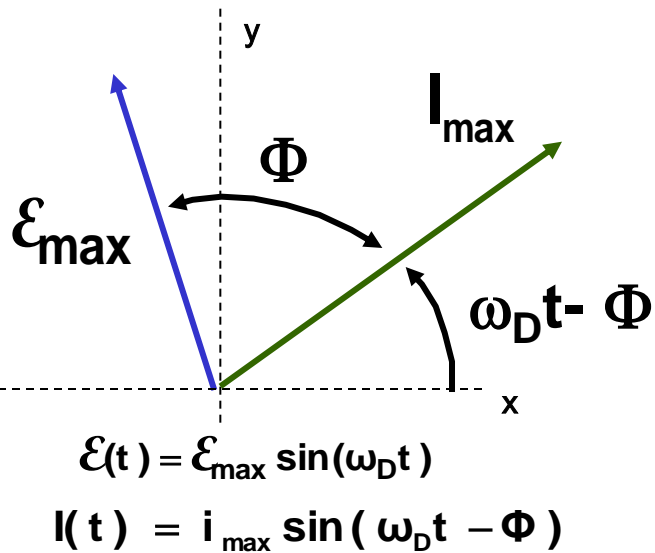Show current and potentials as vectors rotating at frequency ω_D




- The *measured instantaneous* values of $i(t)$ and $\mathcal{E}(t)$ are *projections* of the phasors on the y-axis.
- The lengths of the vectors are the *peak* amplitudes.
- $\Phi \equiv$ “phase angle” measures when peaks pass
- Φ and $\omega_D t$ are independent
- Current is the same (phase included) everywhere in a single branch of any circuit.
- EMF $\mathcal{E}(t)$ applied to the circuit can lead or lag the current by a phase angle Φ in the range $[-\pi/2, +\pi/2]$.

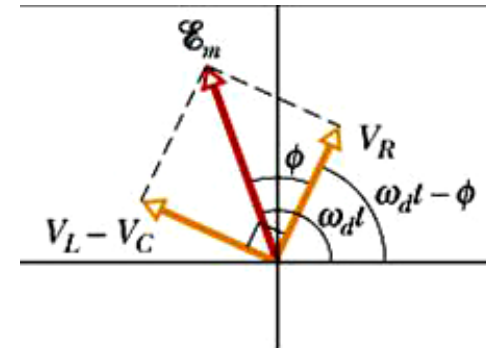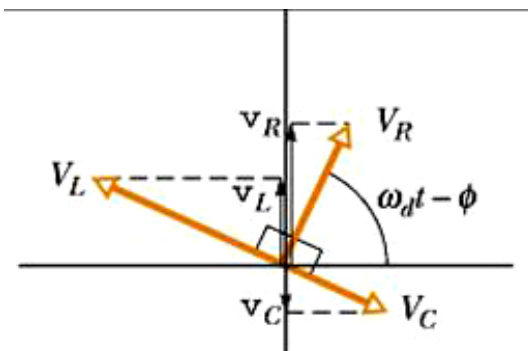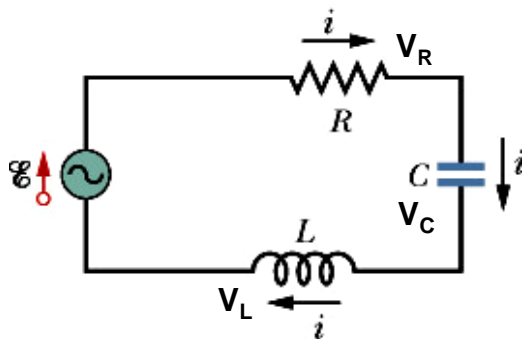Series LCR circuit: Relate internal voltage drops to phase of the current



- Voltage across R is in phase with the current.
- Voltage across C lags the current by 90° .
- Voltage across L leads the current by 90°

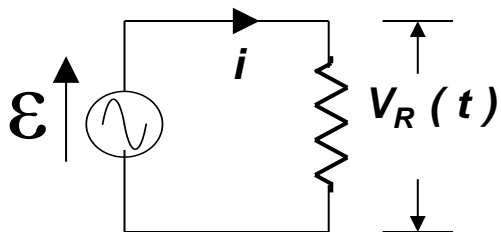AC circuit, resistance only → current and voltage in phase



Kirchoff loop rule: $\epsilon - V_R(t) = 0$

→ $V_R(t) = \epsilon(t) = \epsilon_M \sin(\omega_D t)$


Current $i_R(t) = i_{Rmax} \sin(\omega_D t - \Phi)$

Voltage drop across R: $V_R(t) \equiv i_R(t)R$ (definition of resistance)


$$\frac{\epsilon_m}{i_R} \equiv R$$

$$\therefore \Phi = 0$$

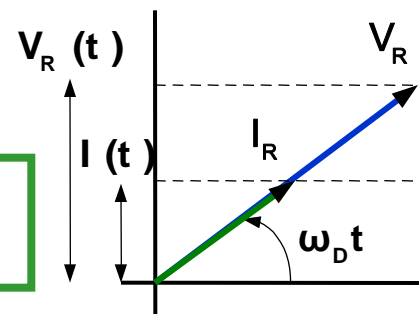Peak current and peak voltage are in phase in a purely resistive part of a circuit, rotating at the driving frequency ω_D



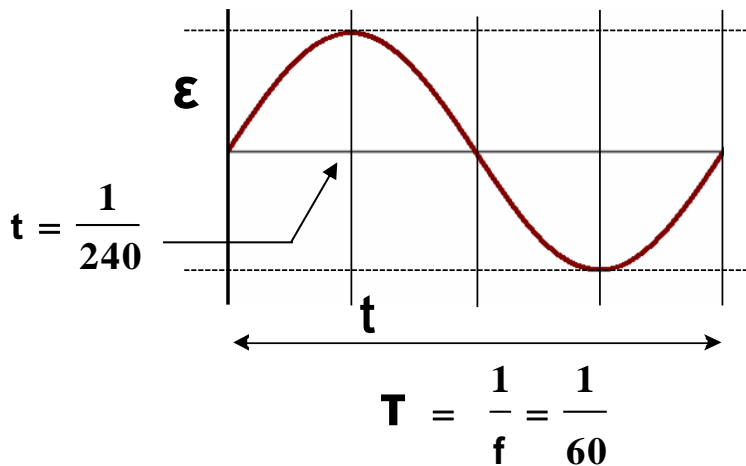Example $\epsilon_M = 10V$, $f = 60Hz$ applied to a 20Ω Resistor. Find the current $i(t)$ at $t = \frac{1}{240}$ s



ϵ_M $\omega_D = 2\pi f = 120\pi$ $\tau = 1/60$ s. $t = \tau/4$

$$i(t) = i_{Rmax} \sin(\omega_D t) = \frac{\epsilon_m}{R} \sin(120\pi \cdot 1/240)$$

$$i(t) = \frac{10}{20} \sin \frac{\pi}{2} = \frac{1}{2} \text{ A}$$

Capacitance-only AC circuit: current leads voltage by $\pi/2$

Kirchoff loop rule: $\epsilon(t) - V_C(t) = 0$

$\Rightarrow V_C(t) = V_{Cmax} \sin(\omega_D t); \quad V_{Cmax} \equiv \epsilon_m$

Charge: $Q(t) = C V_C(t) = C V_{Cmax} \sin(\omega_D t);$

Current: $i_C(t) = \frac{dQ(t)}{dt} = \omega_D C V_{Cmax} \cos(\omega_D t) \equiv i_{Cmax} \sin(\omega_D t - \Phi)$

Note: $\cos(\omega_D t) = \sin(\omega_D t + \frac{\pi}{2})$

so...phase angle $\Phi = -\pi/2$ for capacitor

$V_{Cmax} \equiv i_{Cmax} X_C$ (recall $V_R = i_R R$)

Reactances are ratios of peak values





Definition:
capacitive reactance

$X_C \equiv \frac{1}{\omega_D C}$ (Ohms)

Current leads the voltage by $\pi/2$ in a pure capacitive part of a circuit (Φ negative)

$\therefore i_C(t) = \frac{V_{Cmax}}{X_C} \sin(\omega_D t + \frac{\pi}{2})$

Phasor Picture

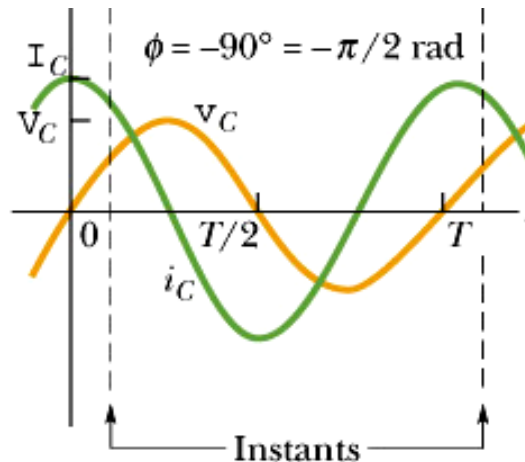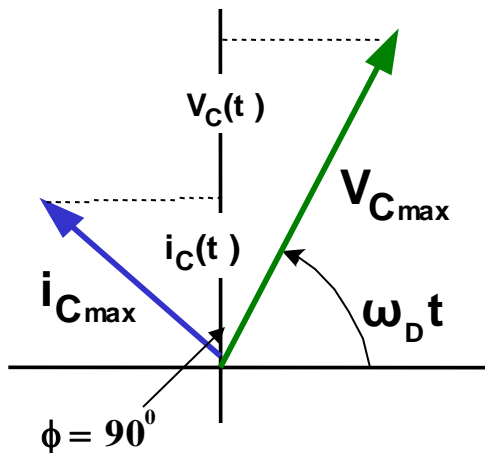

Capacitive Reactance

limiting cases

- $\omega \rightarrow 0$: Infinite reactance. DC blocked. C acts like broken wire.
- $\omega \rightarrow$ infinity: Reactance is zero. Capacitor acts like a simple wire

Inductance-only AC circuit: current lags voltage by $\pi/2$

Kirchoff loop rule: $\mathcal{E}(t) + V_L(t) = 0$

➔ $V_L(t) = -\mathcal{E}_m \sin(\omega_D t); \quad \mathcal{E}_m \equiv V_{Lmax}$

Faraday Law: $V_L(t) = -L \frac{di_L}{dt} \Rightarrow \frac{di_L}{dt} = -\frac{V_L(t)}{L}$

Current: $i_L(t) = \int di_L = \frac{V_{Lmax}}{L} \int \sin(\omega_D t) dt = -\frac{V_{Lmax}}{\omega_D L} \cos(\omega_D t) \equiv i_{Lmax} \sin(\omega_D t - \Phi)$

Note: $\cos(\omega_D t) = -\sin(\omega_D t - \frac{\pi}{2})$

so...phase angle $\Phi = +\pi/2$ for inductor

$V_{Lmax} \equiv i_{Lmax} X_L$



Reactances are ratios of peak values

Definition:
inductive reactance $X_L \equiv \omega_D L$ (Ohms)

Current lags the voltage by $\pi/2$ in a pure inductive part of a circuit (Φ positive)

$i_{Lmax}(t) = \frac{V_{Lmax}}{X_L} \sin(\omega_D t - \frac{\pi}{2})$

Phasor Picture

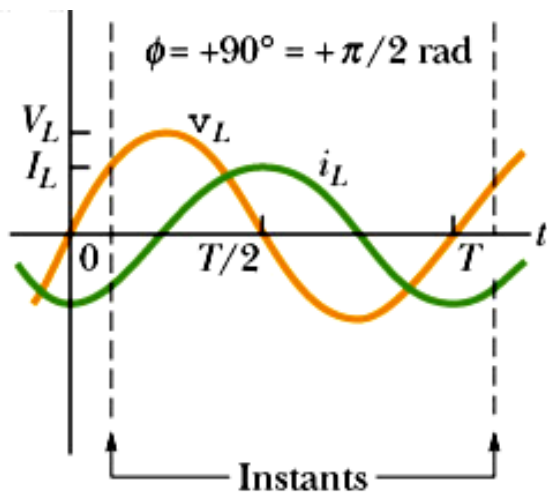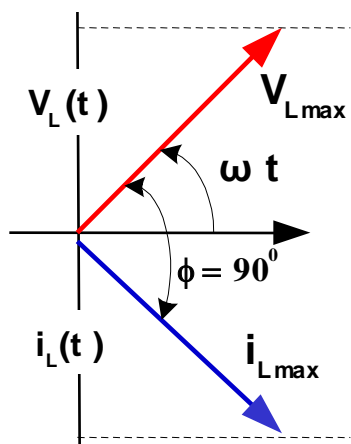


Inductive Reactance limiting cases

- $\omega \rightarrow 0$: Zero reactance. Inductance acts like a wire.
- $\omega \rightarrow$ infinity: Infinite reactance. Inductance acts like a broken wire.

Current & voltage phases in pure R, C, and L circuits


Current is the same everywhere in a single branch (including phase)
 Phases of voltages in elements are referenced to the current phasor

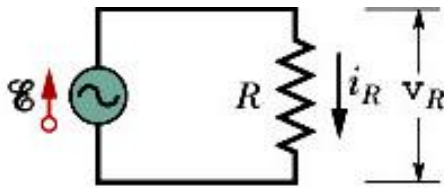- Apply sinusoidal voltage $\mathcal{E}(t) = \mathcal{E}_m \sin(\omega_D t)$
- For pure R, L, or C loads, phase angles are $0, \pi/2, -\pi/2$
- "Reactance" means ratio of **peak voltage** to **peak current** (generalized resistances).




V_R & i_R in phase
 Resistance

$$V_{\max} / i_R \equiv R$$

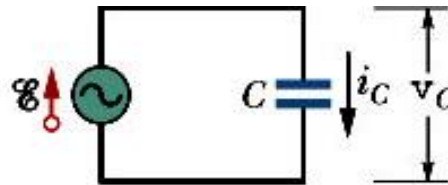




V_C lags i_C by $\pi/2$
 Capacitive Reactance
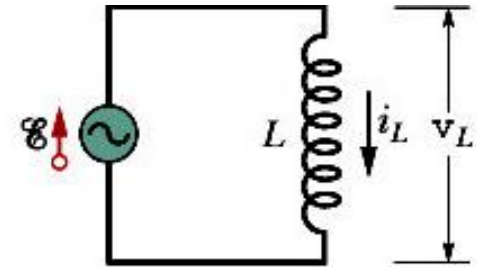
$$V_{\max} / i_C \equiv X_C = \frac{1}{\omega_D C}$$




V_L leads i_L by $\pi/2$
 Inductive Reactance
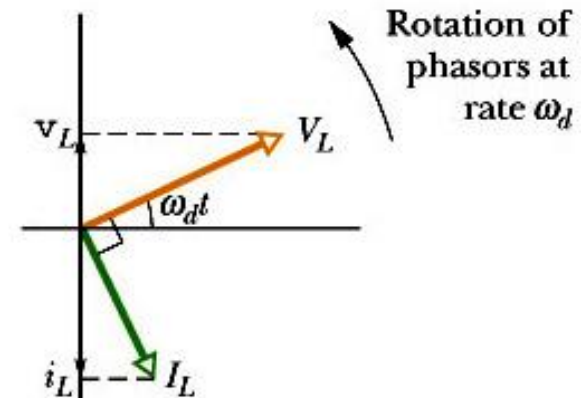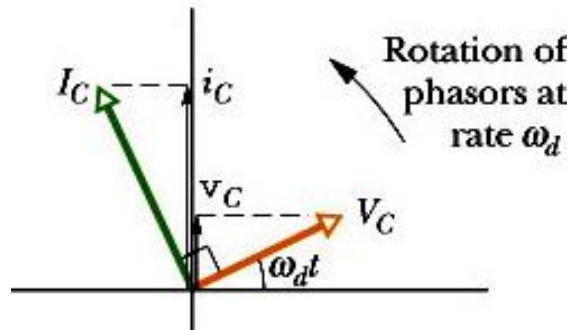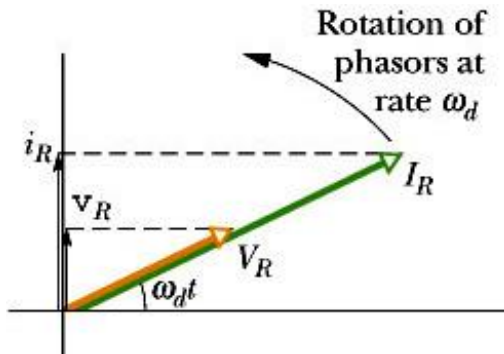
$$V_{\max} / i_L \equiv X_L = \omega_D L$$



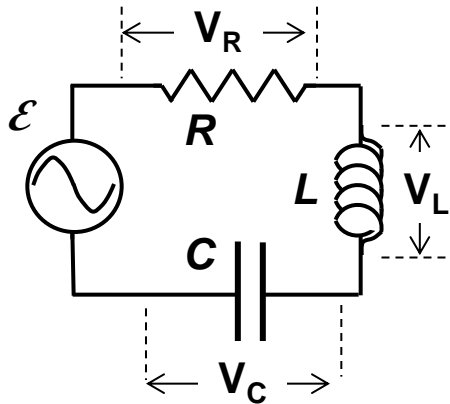Series LCR circuit driven by an external AC voltage



Apply EMF:

$$\mathcal{E}(t) = \mathcal{E}_{\max} \sin(\omega_D t) \quad \omega_D \text{ is the driving frequency}$$


The current $i(t)$ is the same everywhere in the circuit

$$i(t) = i_{\max} \sin(\omega_D t - \Phi)$$

- Same frequency dependence as $\mathcal{E}(t)$ but...
- Current leads or lags $\mathcal{E}(t)$ by a constant phase angle Φ
- Same phase for the current in \mathcal{E} , R, L, & C


Phasors all rotate CCW at frequency ω_D

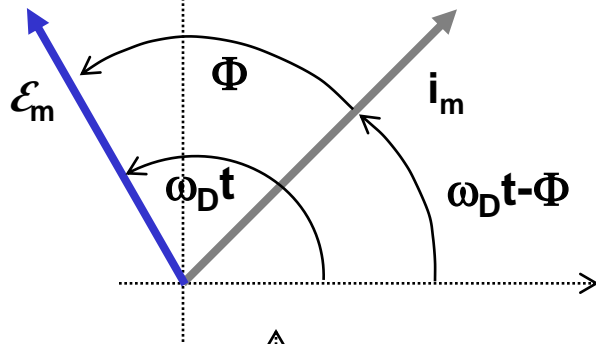- Lengths of phasors are the peak values (amplitudes)
- The “y” components are the measured values.



Plot voltages in components with phases relative to current phasor i_m :

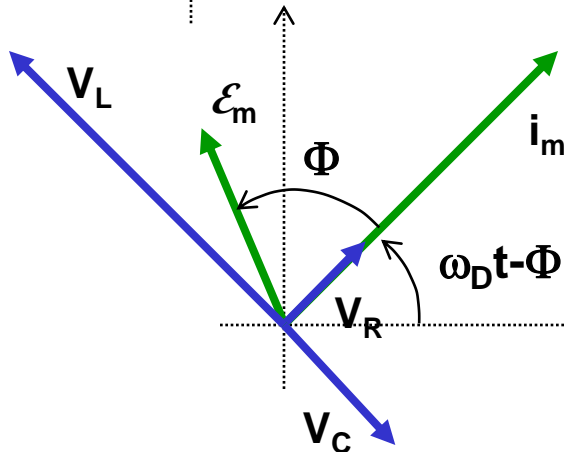- V_R has same phase as i_m $V_R = i_m R$
- V_C lags i_m by $\pi/2$ $V_C = i_m X_C$
- V_L leads i_m by $\pi/2$ $V_L = i_m X_L$



Kirchoff Loop rule for potentials (measured along y)

$$\vec{\mathcal{E}}(t) - \vec{V}_R(t) - \vec{V}_L(t) - \vec{V}_C(t) = 0$$

$$\vec{\mathcal{E}}_m = \vec{V}_R + (\vec{V}_L + \vec{V}_C) \quad \vec{V}_C \text{ lags } \vec{V}_L \text{ by } 180^\circ$$

↗ along i_m
↖ perpendicular to i_m


Summary: Lecture 13/14 Chapter 31 - LCR & AC Circuits, Oscillations

LC OSCILLATOR

$$q(t) = q_0 \cos(\omega t) \quad \omega = (LC)^{-1/2} \quad U_{TOT} = U_B + U_E = \frac{1}{2} L \dot{q}^2 + \frac{q^2}{2C}$$

$$I_m = q_0 \omega$$

$$i(t) = -q_0 \omega \sin(\omega t)$$

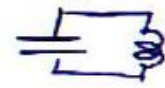

$$\frac{dU_{TOT}}{dt} = 0$$

DAMPED LC OSCILLATOR

$$q(t) = e^{-Rt/2L} \cos(\omega' t + \phi) \quad \omega' = [\omega^2 - (\frac{R}{2L})^2]^{1/2} \quad \omega = \sqrt{\frac{1}{LC}}$$

UNDETERMINED




AC CIRCUITS: APPLY EMF: $\mathcal{E}(t) = \mathcal{E}_0 \sin(\omega t)$ CURRENT: $i(t) = I_m \sin(\omega t + \phi)$

ϕ = PHASE ANGLE RELATES PEAKS


PHASE & AMPLITUDE RELATIONS

RESISTOR R	Resistance R	I_m, V_R INPHASE	$V_R = I R$
CAPACITOR C	$X_C = (\omega C)^{-1}$	V_C LAGS I_m by $\pi/2$	$V_C = I_C X_C$
INDUCTOR L	$X_L = \omega L$	V_L LEADS I_m by $\pi/2$	$V_L = I_L X_L$

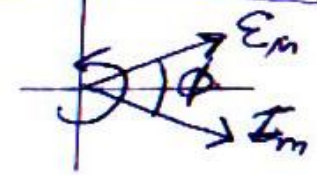

SERIES LCR CIRCUIT:

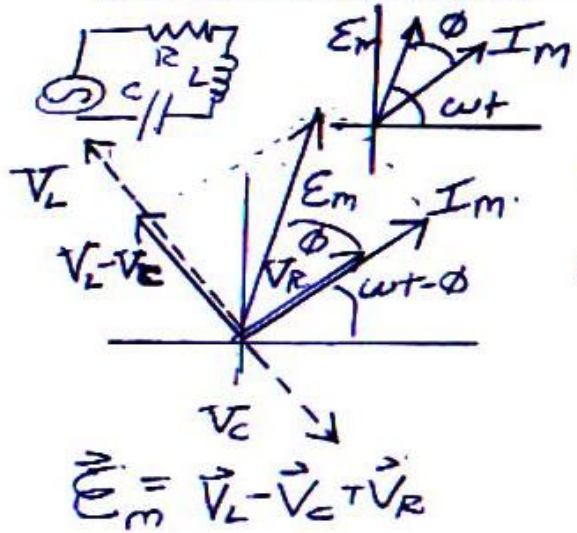
APPLY LOOP RULE, ALSO CURRENT THE SAME EVERYWHERE



$$|E_m| = [V_R^2 + (V_L - V_C)^2]^{1/2} = |I_m| Z \leftarrow \text{IMPEDANCE}$$

$$Z = [R^2 + (X_L - X_C)^2]^{1/2} \quad \tan \phi = \frac{V_L - V_C}{V_R} = \frac{X_L - X_C}{R}$$

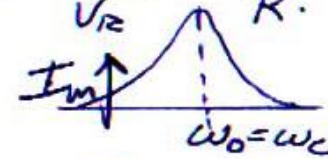RESONANCE AT $\omega_0 = \omega = 1/\sqrt{LC}$



AVERAGING POWER

$$P_{AV} = I_{RMS}^2 R$$

$$I_{RMS} = I_m / \sqrt{2}$$

$$E_{RMS} = E_m / \sqrt{2}$$

ETC.

POWER FACTOR


$$P_{AV} = E_{RMS} I_{RMS} \cos \phi$$

$$= E_{RMS} I_{RMS} \cos \phi$$

$$\cos \phi = R/Z$$

$$R = Z \cos \phi$$

$$I_{RMS} = \frac{E_{RMS}}{Z}$$

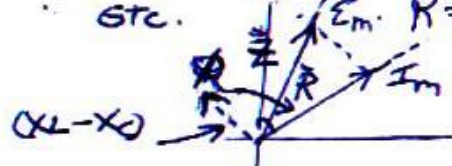

TRANSFORMERS



SAME FLUX IN EACH TURN



$$\frac{N_s}{N_p} = \frac{V_s}{V_p} = \frac{I_p}{I_s}$$

100% EFFICIENCY

Summary: RC and RL circuit results

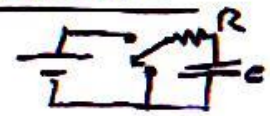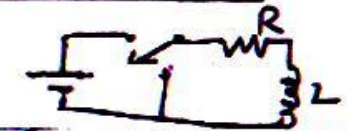RECAP	RC CIRCUITS	LR CIRCUITS
TIME CONSTANT	$\tau_c = RC$ 	$\tau_L = L/R$ 
MEASURE OF CAPACITY	$C \equiv Q/V_c$ GEOMETRY	$L \equiv \frac{N \Phi_B}{I} = \frac{\text{"FLUX LINKAGE"}}{\text{UNIT CURRENT}}$ $\Phi_B = \text{FLUX THROUGH ONE COIL}$
LIMITING VALUES	$Q_{\infty} = CE$	$i_{\infty} = E/R$
LOOP RULE VOLTAGE & DIR.	$V_c = Q/C$	$E_L = -L di/dt$ (FARADAY'S LAW)
EQUATION	$E - R \frac{dQ}{dt} - \frac{Q}{C} = 0$	$E - iR - L \frac{di}{dt} = 0$
GROWTH PHASE	$i(t) = \frac{E}{R} e^{-t/\tau_c}$	$i(t) = \frac{E}{R} (1 - e^{-t/\tau_L})$
SOLUTION	$V_c(t) = -E(1 - e^{-t/\tau_c})$ $V_R(t) = i(t)R$ $Q(t) = Q_{\infty}(1 - e^{-t/\tau_c})$	$V_L(t) = -E e^{-t/\tau_L}$ (BACK EMF) $V_R(t) = i(t)R$
DECAY PHASE	$i(t) = \frac{E}{R} e^{-t/\tau_c}$	$i(t) = \frac{E}{R} e^{-t/\tau_L}$
SOLUTION	$V_c(t) = E e^{-t/\tau_c}$ $Q(t) = CE e^{-t/\tau_c}$	$V_L(t) = i(t)R = E e^{-t/\tau_L}$