

Electricity and Magnetism

Lecture 07 - Physics 121

Current, Resistance, DC Circuits: Y&F Chapter 25 Sect. 1-5

Kirchhoff's Laws: Y&F Chapter 26 Sect. 1

- Circuits and Currents
- Electric Current i
- Current Density J
- Drift Speed
- Resistance, Resistivity, Conductivity
- Ohm's Law
- Power in Electric Circuits
- Examples
- Kirchhoff's Rules applied to Circuits
- EMF's - "Pumping" Charges
- Work, Energy, and EMF
- Simple Single Loop and Multi-Loop Circuits
- Summary

Electric Current: Net charge crossing a surface per unit time

$$i \equiv \frac{dq}{dt} \quad \text{or} \quad dq \equiv i dt \quad \therefore \quad q(t) = \int_0^t i(t') dt' = i \times t \quad (\text{if } i \text{ is constant})$$


Units: 1 Ampere = 1 Coulomb per second

Convention: flow is from + to - as if free charges are +

Charge / current is conserved - charge does not pile up or vanish


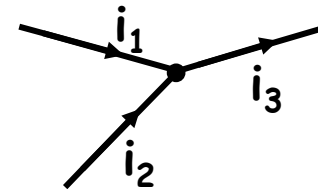
$$\text{At any junction} \quad \sum i_{\text{in}} = \sum i_{\text{out}}$$




$$i_1 + i_2 = i_3$$

kirchhoff's
Rules:
(summary)

- Junction Rule: \sum currents in = \sum currents out at any junction
- Voltage Rule: $\sum \Delta V$'s = 0 for any closed path

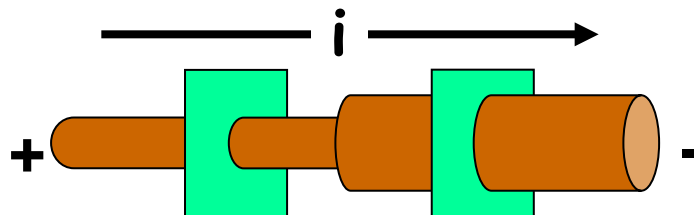Current is the same across each cross-section of a wire



Current density \underline{J} may vary
 $[J] = \text{current/area}$

Energy
in a circuit:

- EMFs provide energy (electro-motive force)
- Resistances dissipate energy as heat
- Capacitances store energy in \underline{E} field
- Inductances store energy in \underline{B} field

CURRENT CONSERVATION EXAMPLE:


Find the unknown current i

Name the junctions

Name the links by the junctions they connect

Apply the
junction rule:
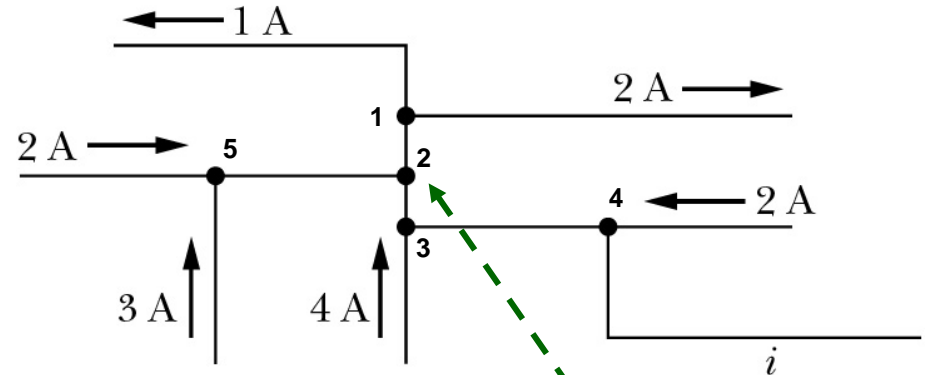
$$\sum i_{\text{in}} = \sum i_{\text{out}}$$



Using Junction 1:

$$i_{1,2} = 2 \text{ A} + 1 \text{ A} = 3 \text{ A} \quad \text{into junction 1, out of junction 2}$$

Using Junction 5:

$$i_{5,2} = 2 \text{ A} + 3 \text{ A} = 5 \text{ A} \quad \text{out of junction 5, into junction 2}$$

Using Junction 2:


$$i_{2,3} + i_{1,2} = i_{5,2} = 5 \text{ A} \quad \text{out of junction 2, into junction 3}$$

Using Junction 3:

$$i_{3,4} = 4 \text{ A} + 2 \text{ A} = 6 \text{ A} \quad \text{out of junction 3, into junction 4}$$

Using Junction 4:

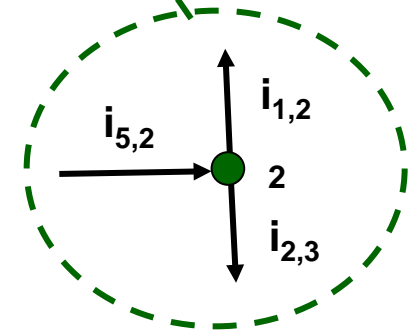
$$i = 6 \text{ A} + 2 \text{ A} = 8 \text{ A} \quad \text{out of junction 4, to the right}$$



Try this one yourself


7-1: What is the current in the wire section marked i ?

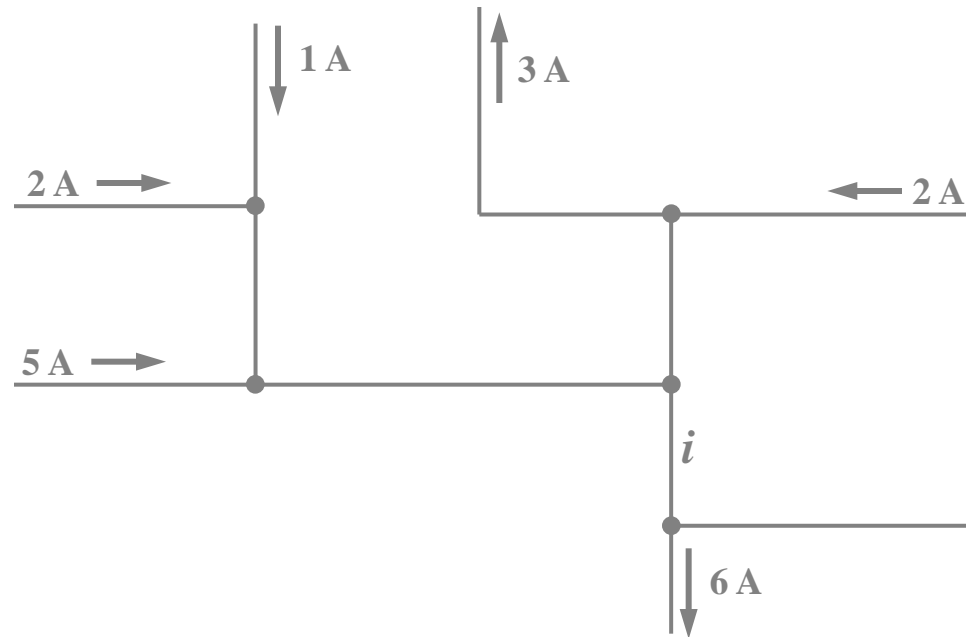- A. 1 A.
- B. 2 A.
- C. 5 A.
- D. 7 A.
- E. Cannot determine from information given.




$$\sum i_{\text{in}} = \sum i_{\text{out}}$$

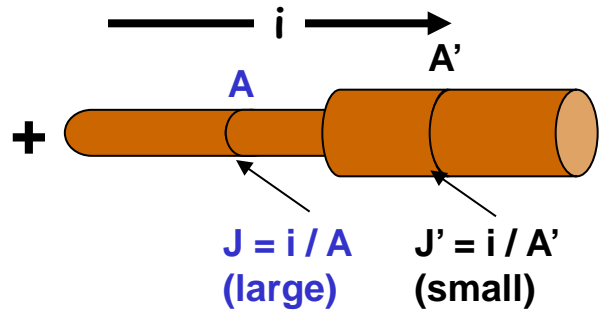Current density \underline{J} : Current / Unit Area (Vector)



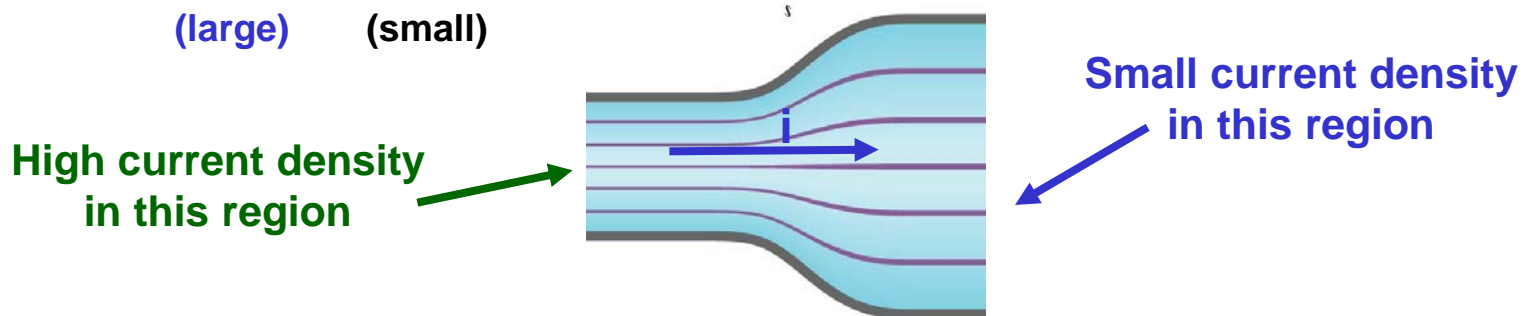Same current crosses larger or smaller Surfaces, current density J varies



For uniform density $i = J A$ or $J = i/A$ units: Amperes/m²


$$di \equiv \vec{J} \cdot \hat{n} dA$$

$$i = \int_{\text{area}} \vec{J} \cdot d\vec{A}$$


What makes current flow?

$$\vec{J} \propto \vec{E} \quad \vec{J} = \sigma \vec{E}$$

E field in solid wire drives current.

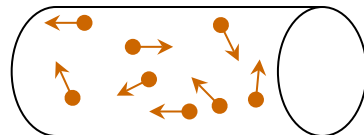

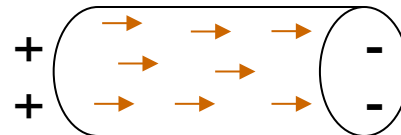APPLIED FIELD = 0
Random motion
flow left = flow right



APPLIED FIELD NOT ZERO
Moving charges collide with fixed ions and flow with drift velocity

Do charges in a current keep accelerating as they flow?

Electrons collide with ions, impurities, etc. causing resistance


Move at constant drift speed v_D :

- Thermal motions (random motions) have speed $v_{th} \approx 10^6 \text{ m/s}$ ($\frac{3}{2} k_{\text{Boltz}} T$)
- Drift speed is tiny compared with thermal motions.
- Drift speed in copper is $10^{-8} - 10^{-4} \text{ m/s}$.

$$\mathbf{J} \propto \mathbf{E} \quad \mathbf{J} = \sigma \mathbf{E}$$

For $E = 0$: no current,
 $v_D = 0$, $J = 0$, $i = 0$

For E not = 0
(battery voltage not 0):

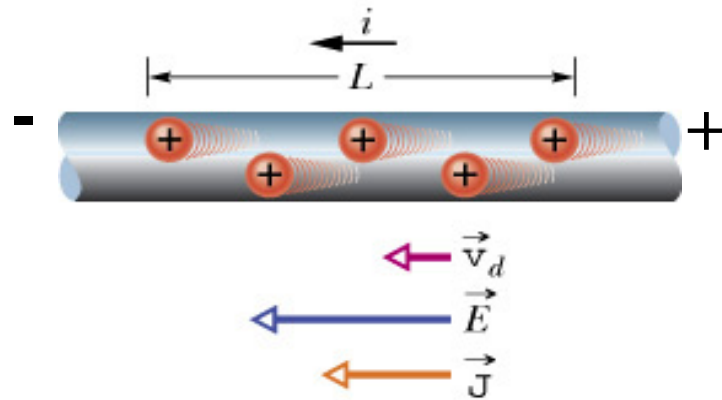

$n \equiv$ density of charge carriers Units : #/volume

$n v_D =$ # of charge carriers crossing unit area per unit time

$$\mathbf{J} = q n v_D = \text{net charge crossing area } A \text{ per unit time}$$

Note: for electrons, q & v_D are both reversed $\rightarrow J$ still to left
 $|q| = e = 1.6 \times 10^{-19} \text{ C}$.

EXAMPLE: Calculate the current density J_{ions} for ions in a gas

Assume:

- Doubly charged positive ions
- Density $n = 2 \times 10^8$ ions/cm³
- Ion drift speed $v_d = 10^5$ m/s

Find J_{ions} - the current density for the ions only (forget $J_{\text{electrons}}$)

$$J = qn v_D = \underbrace{2 \times 1.6 \times 10^{-19}}_{\text{coul/ion}} \times \underbrace{2 \times 10^8}_{\text{ions/cm}^3} \times \underbrace{10^5}_{\text{m/s}} \times \underbrace{10^6}_{\text{cm}^3/\text{m}^3}$$

$$\therefore J = 6.4 \text{ A./m}^2$$

Increasing the Current

7-2: When you increase the current in a wire, what changes and what is constant?


- A. The density of charge carriers stays the same, and the drift speed increases.
- B. The drift speed stays the same, and the number of charge carriers increases.
- C. The charge carried by each charge carrier increases.
- D. The current density decreases.

$$\mathbf{J \propto E \quad J = \sigma E}$$

$$\mathbf{J = qn v_D}$$



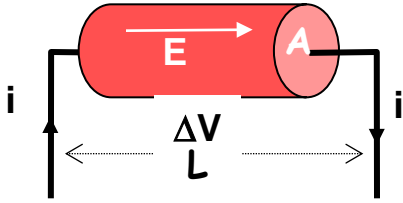Resistance: Determines how much current flows through a device in response to a given potential difference.



$$R \equiv \frac{\Delta V}{i} \quad \text{units: } 1 \text{ Ohm} \equiv 1 \Omega = 1 \text{ volt/ampere}$$

R depends on the material & geometry


Note: $C = Q/\Delta V$ - inverse to R

Apply voltage to a conducting wire.

- Very large current so R is small.

Apply voltage to a poor conductor material like carbon

Tiny current so R is very large.

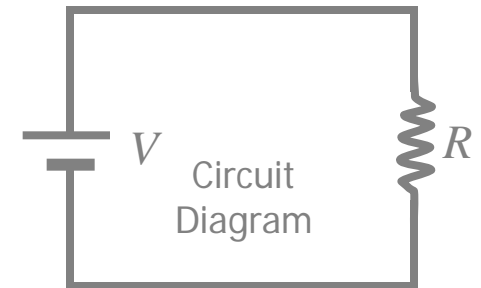

Resistivity "ρ" : Property of a material itself

(as is dielectric constant). Does not depend on dimensions

- The resistance of a device depends on resistivity ρ and also depends on shape
- For a given shape, different materials produce different currents for same ΔV
- Assume cylindrical resistors


$$R \equiv \text{resistance} = \frac{\rho L}{A}$$

$$\rho \equiv \text{resistivity} = \frac{RA}{L} \quad \text{for a resistor}$$

For insulators: $\rho \rightarrow \text{infinity}$

resistivity units: Ohm-meters $\equiv \Omega \cdot \text{m}$

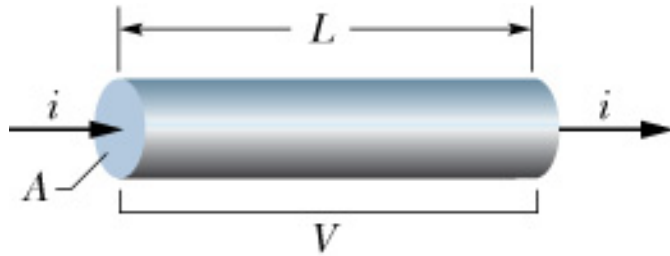Calculating resistance, given the resistivity



resistivity ρ

resistance R

$$R = \frac{\rho L}{A}$$

proportional to length

inversely proportional to cross section area

EXAMPLE:

Find R for a 10 m long iron wire, 1 mm in diameter

$$R = \frac{\rho L}{A} = \frac{9.7 \times 10^{-8} \Omega \cdot \text{m} \times 10 \text{ m}}{\pi \times (10^{-3} / 2)^2 \text{ m}^2} = 1.2 \Omega$$

Find the potential difference across R if $i = 10 \text{ A}$. (Amperes)

$$\Delta V = iR = 12 \text{ V}$$

EXAMPLE:

Find resistivity of a wire with $R = 50 \text{ m}\Omega$,
diameter $d = 1 \text{ mm}$, length $L = 2 \text{ m}$

$$\rho = \frac{RA}{L} = \frac{50 \times 10^{-3} \Omega \times 10 \text{ m}}{2 \text{ m}} \times \pi \left(\frac{10^{-3}}{2} \right)^2 = 1.96 \times 10^{-8} \Omega \cdot \text{m}$$

Use a table to identify material. Not Cu or Al, possibly an alloy

Resistivity depends on temperature:

- Resistivity depends on temperature: Higher temperature \rightarrow greater thermal motion \rightarrow more collisions \rightarrow higher resistance.

SOME SAMPLE RESISTIVITY VALUES	ρ in $\Omega \cdot m$ @ 20° C.	Reference Temperature
	1.7×10^{-8} copper	
	9.7×10^{-8} iron	
	$2.5 \times 10^{+3}$ pure silicon	


Simple model of resistivity: α = temperature coefficient

Change the temperature from
reference T_0 to T
Coefficient α depends on the material

$$\rho = \rho_0(1 + \alpha(T - T_0))$$

$\alpha \equiv$ temperature coefficient

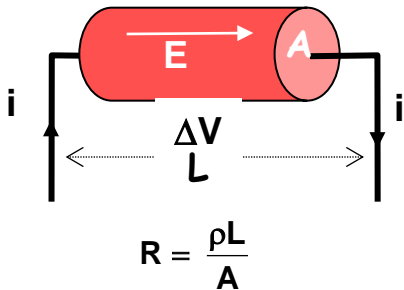Conductivity is the reciprocal of resistivity



Definition:


$$\sigma \equiv \frac{1}{\rho} \quad \therefore \mathbf{J} = \sigma \mathbf{E} \quad \text{units: "mho"} \equiv (\Omega \cdot m)^{-1}$$

$$\Delta V = \mathbf{E}L = iR = \mathbf{J}AR = \mathbf{J}\rho L \quad \therefore \mathbf{E}/\mathbf{J} = \rho$$

Current Through a Resistor

7-3: What is the current through the resistor in the following circuit, if $V = 20\text{ V}$ and $R = 100\ \Omega$?

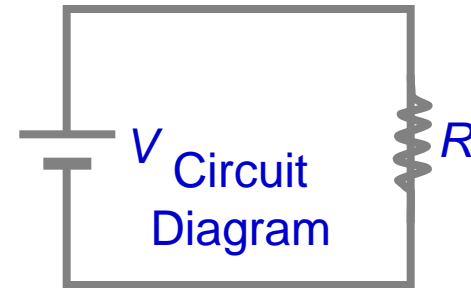- A. 20 mA.
- B. 5 mA.
- C. 0.2 A.
- D. 200 A.
- E. 5 A.



$$\Delta V = iR$$


Current Through a Resistor

7-4: If the current is doubled, which of the following might also have changed?

- A. The voltage across the resistor doubles.**
- B. The resistance of the resistor doubles.**
- C. The voltage in the wire between the battery and the resistor doubles.**
- D. The voltage across the resistor drops by a factor of 2.**
- E. The resistance of the resistor drops by a factor of 2.**



$$\Delta V = iR$$

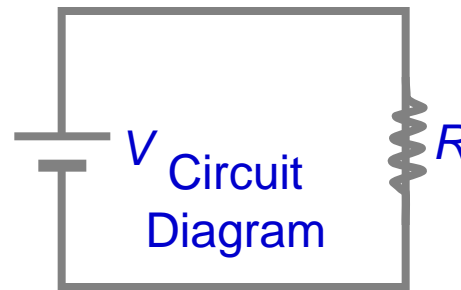


Resistivity of a Resistor

$$R = \frac{\rho L}{A}$$

7-5: Three resistors are made of the same material, with sizes in mm shown below. Rank them in order of total resistance, greatest first.

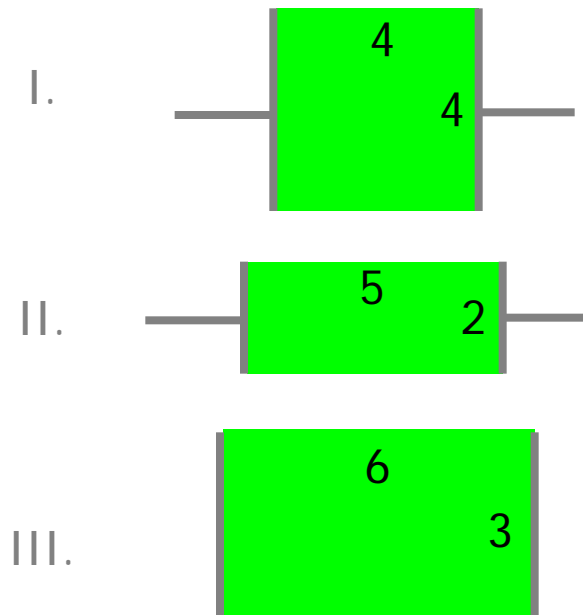- A. I, II, III.
- B. I, III, II.
- C. II, III, I.
- D. II, I, III.
- E. III, II, I.



Each has
square
cross-section


Ohm's Law and Ohmic materials (a special case)

Definitions of resistance: $R \equiv V/i$ but R could depend on applied V
 $\sigma \equiv 1/\rho = J/E$ but ρ could depend on E

Definition of OHMIC conductors and devices:


- Ratio of voltage drop to current is constant – it does not depend on applied voltage i.e., current is proportional to applied V
- Resistivity does not depend on magnitude or direction of applied voltage

Ohmic Materials
e.g., metals, carbon,...

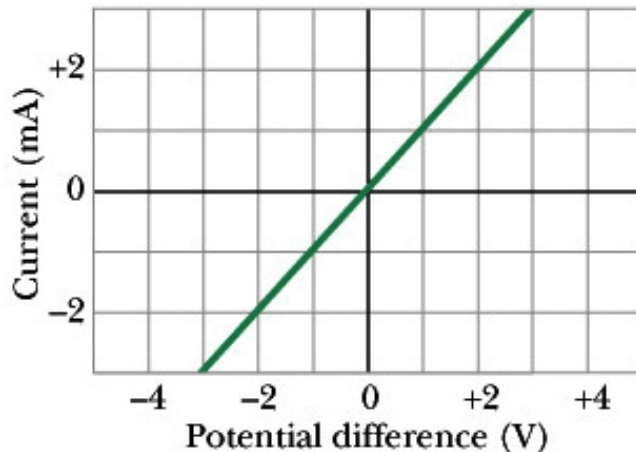

constant slope = $1/R$

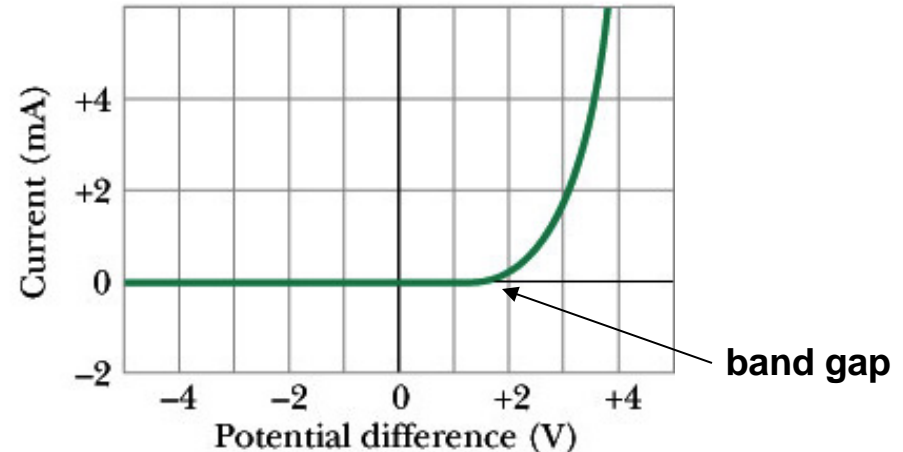
Non-Ohmic Materials
e.g., semiconductor devices



varying slope = $1/R$

OHMIC CONDITION $\frac{1}{R} \equiv \frac{di}{dV}$ **is CONSTANT**

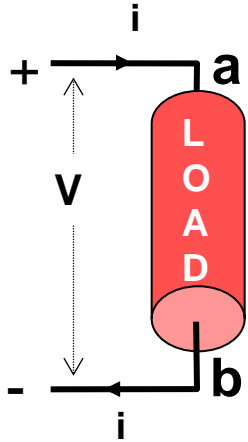Power is dissipated in resistive circuits



- Apply voltage drop V across load
- Current flows through load which dissipates energy
- An EMF (e.g., a battery) does work, holding V and current i constant by expending potential energy

As charge dq flows from a to b it loses P.E. = dU

- potential is PE / unit charge
- charge = current x time




$$dU = V dq = Vi dt$$

$$\text{Power dissipation} = P \equiv \frac{dU}{dt} = Vi \quad [\text{Watts}] \text{ for any load}$$

$$V = iR \Rightarrow P = i^2 R = V^2 / R \quad \text{resistors only}$$

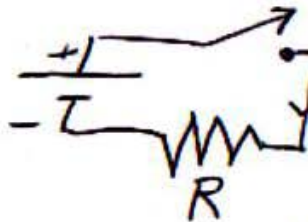EXAMPLE: Space heater: Find rate of converting electrical energy to heat



$$V = 120 \text{ Volts}$$

$$R = 14 \Omega$$

$$\text{FIND POWER} = \frac{V^2}{R} = 1 \text{ KW}$$

$$\text{KW} \equiv \text{KILOWATT} = 1000 \text{ WATTS}$$

NOW, HOW MUCH DOES IT COST PER DAY
TO RUN, IF 1 KWH = 12¢

$$\text{COST} = \frac{\text{Power} \times \text{Time} \times \text{Unit Energy Cost}}{\text{Cost}} = 1 \text{ KW} \times 24 \text{ Hours} \times 0.12 / \text{KWh} = 2.88$$

EXAMPLE:

A 47Ω resistor is rated for up to 10 watts. What's the max voltage.

$$P_{\max} = V_{\max}^2 / R \quad V_{\max} = \sqrt{P_{\max} R} = 21.6 \text{ Volts}$$

EXAMPLE:

A 100 watt light bulb is rated for 120V.

Find i in the light

$$P = iV \quad i = P/V = \frac{100 \text{ W}}{120 \text{ V}} = 0.83 \text{ A}$$

EXAMPLE:

10 Amps flows in an iron wire. 1m long and 1mm in diameter.

a) How much power is dissipated

$$P = i^2 R \quad R = \frac{\rho L}{A} = \frac{9.7 \times 10^{-8} \times 1 \text{ m}}{\pi \times \frac{1}{4} \times 10^{-6} \text{ m}^2} =$$

$$R = 0.123 \Omega$$


$$P = 100 \times 0.123 \Omega = 12.3 \text{ Watts}$$

b) What voltage is across the wire.

$$P = iV \quad V = P/i = 1.23 \text{ Volts}$$

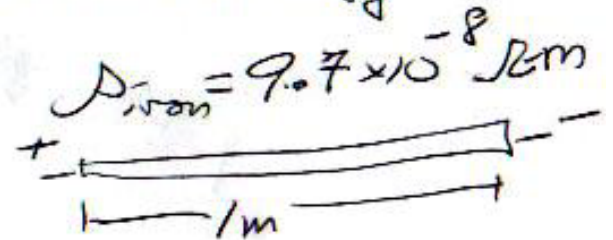c) What should V be to dissipate 100 watts?

$$P = \frac{V^2}{R} \quad V = \sqrt{P R} = \sqrt{100 \times 0.123 \Omega} = 3.5 \text{ Volts}$$



Ohmic and non-ohmic conductors

SUPERCONDUCTORS: At very low temperatures (~4 K) some conductors lose all resistance. Once you start current flowing, it will continue to flow “forever,”


- The current becomes enormous once the applied voltage exceeds a small value.

7-6: The three plots show voltage vs. current (so the slope is R) for three kinds of devices. Identify the devices in order appearing in charts I, II, III?

- A. Resistor, superconductor, diode
- B. Diode, superconductor, resistor
- C. Resistor, diode, superconductor
- D. Diode, resistor, superconductor
- E. Superconductor, resistor, diode



$$R \equiv \frac{\Delta V}{\Delta i}$$

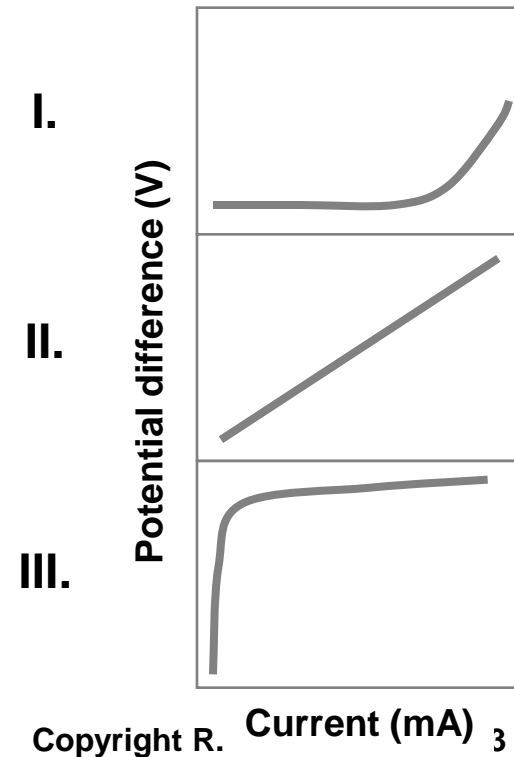

Circuit analysis with resistances and EMFs

GENERAL ANALYSIS METHOD: kirchhoff'S LAWS or RULES


Junction Rule $\sum i_{in} = \sum i_{out}$ Charge conservation

Loop Rule $\sum \Delta V = 0$ (closed loop) Energy conservation

CIRCUIT ELEMENTS:

- PASSIVE: RESISTANCE, CAPACITANCE, INDUCTANCE
- ACTIVE: EMF's (SOURCES OF POTENTIAL DIFFERENCE AND ENERGY)

JUNCTIONS and BRANCHES

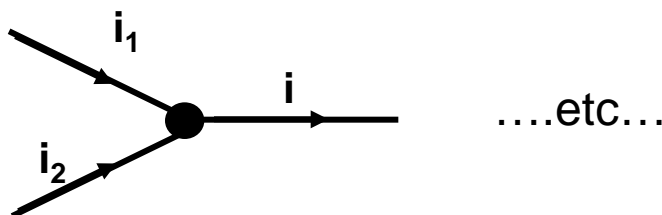

RESISTANCE:


$$R \equiv \frac{\Delta V}{i}$$

$$R = \rho \frac{L}{A} \quad \rho = \text{resistivity}$$

POWER:

$$P = \frac{dW}{dt} = -\frac{dU}{dt} = iV \quad P = i^2 R \text{ (resistor)}$$


OHM'S LAW:

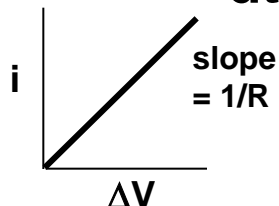

R is independent of ΔV or i

EMFs “pump” charges to higher energy

- EMFs move charges from low to high potential (potential energy).
- EMF's (*electromotive force*) such as batteries supply energy:
 - maintain constant potential at terminals
 - do work $dW = \mathcal{E}dq$ on charges (source of the energy is usually chemical)
 - EMFs are “charge pumps”
- Unit: volts (V). Symbol: script \mathcal{E} .
- Types of EMFs: batteries, electric generators, solar cells, fuel cells, etc.
- DC versus AC

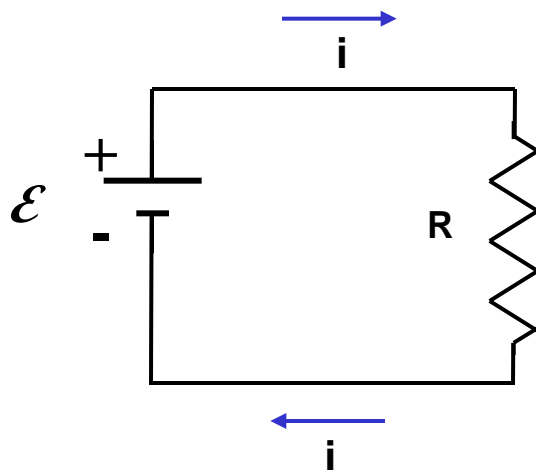

Current flows CW through circuit
from + to - outside of EMF
from - to + inside EMF

$$\mathcal{E} = \frac{\text{work done}}{\text{unit charge}} = \frac{dW}{dq}$$

Power supplied by EMF:

$$P = \text{power} = \frac{dW}{dt}$$

$$dW = \mathcal{E} dq = \mathcal{E} i dt = P dt$$


$$P_{\text{emf}} = \pm \mathcal{E} i = \vec{\mathcal{E}} \circ \vec{i}$$

Power dissipated by resistor:

$$P_R = iV = i^2 R = V^2 / R$$


Ideal EMF device

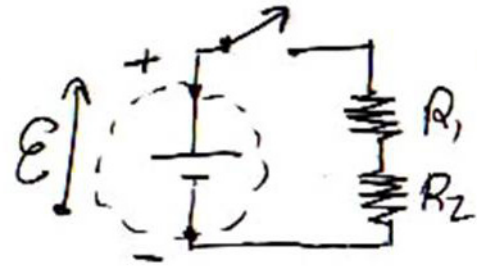- Zero internal battery resistance
- Open switch: $EMF = \mathcal{E}$
no current, zero power
- Closed switch: $EMF \mathcal{E}$ is also applied across load circuit
- Current & power not zero



Real EMF device

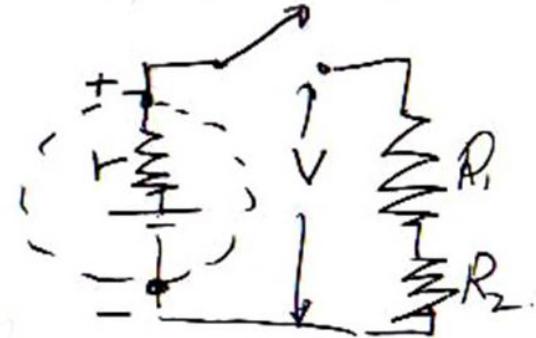- Open switch: $EMF \text{ still} = \mathcal{E}$
- $r =$ internal EMF resistance in series, usually small $\sim 1 \Omega$
- Closed switch:
 - $V = \mathcal{E} - ir$ across load, $P_{\text{ckt}} = iV$
 - Power dissipated in EMF
 $P_{\text{emf}} = i(\mathcal{E} - V) = i^2 r$




$r = \text{small (usually)}$
 $\sim 1 \Omega$

Multiple EMFs

Assume $\mathcal{E}_B > \mathcal{E}_A$ (ideal EMF's)
Which way does current i flow?

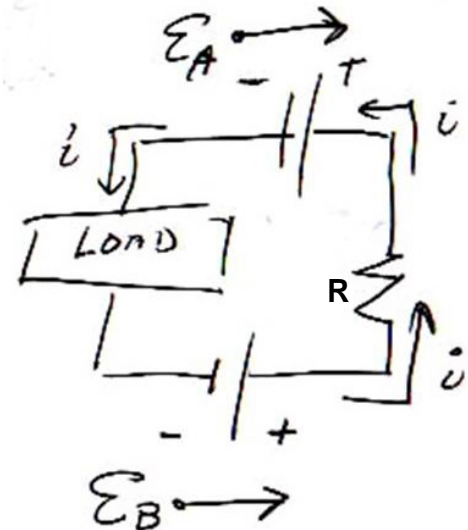
- Apply kirchhoff Laws to find out
- Answer: From \mathcal{E}_B to \mathcal{E}_A
- \mathcal{E}_B does work, loses energy
- \mathcal{E}_A is charged up
- R converts PE to heat
- Load (motor, other) produces motion and/or heat



Generating Circuit Equations with the Kirchhoff Loop Rule

- The algebraic sum of voltage changes = zero around all closed loops through a circuit (including multi-loop)
- Assume either current direction. Expect minus signs when choice is wrong.
- Traverse circuit with or against assumed current direction
- Across resistances, voltage drop $\Delta V = -iR$ if following assumed current direction. Otherwise, voltage change is $+iR$.
- When crossing EMFs from $-$ to $+$, $\Delta V = +\mathcal{E}$. Otherwise $\Delta V = -\mathcal{E}$
- Dot product $\mathbf{i} \cdot \mathbf{\mathcal{E}}$ determines whether power is actually supplied or dissipated

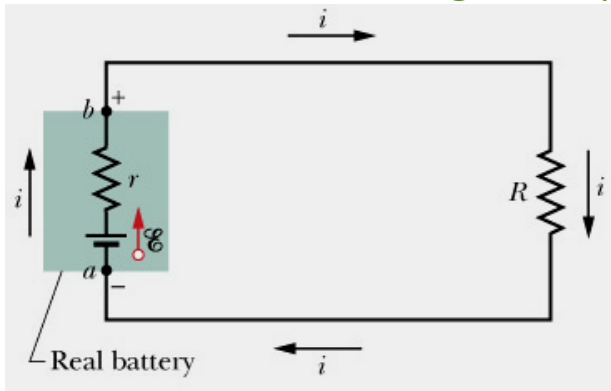EXAMPLE: Single loop circuit with battery (internal resistance r)



Follow circuit from a to b to a, same direction as i

$$\mathcal{E} - ir - iR = 0$$



$$i = \frac{\mathcal{E}}{r + R}$$

Power in External Ckt

$$P = iV = i(\mathcal{E} - ir)$$


$$P = i\mathcal{E} - i^2r$$

circuit
dissipation

battery
drain


battery
dissipation

Potential around the circuit

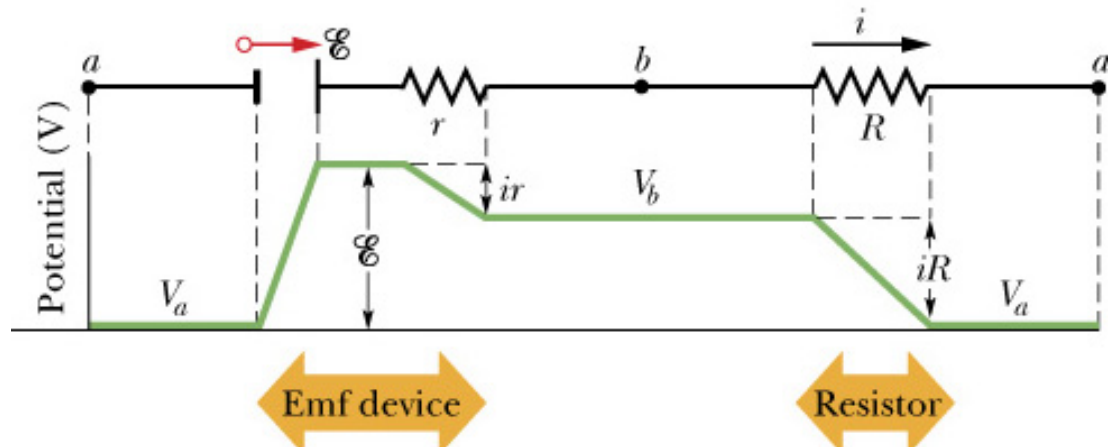

Example: CW or CCW around a single-loop circuit

Assume current direction as shown

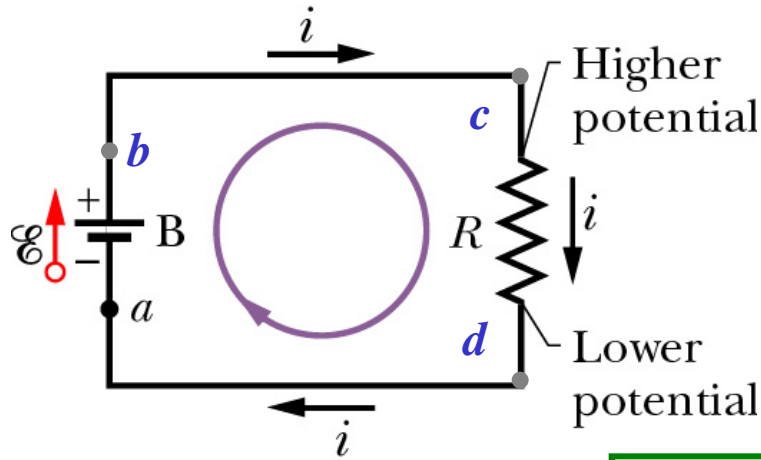

- Traverse clockwise from a:

$$\Delta V_{ba} = V_b - V_a = +\varepsilon$$

$$\Delta V_{cb} = 0$$


$$\Delta V_{dc} = V_d - V_c = -iR$$

$$\Delta V_{ad} = 0$$

$$\sum_{\text{closed loop}} \Delta V = 0 = \varepsilon + 0 - iR + 0$$

$$\begin{aligned} \varepsilon - iR &= 0 \\ i &= \frac{\varepsilon}{R} \end{aligned}$$

SAME RESULT

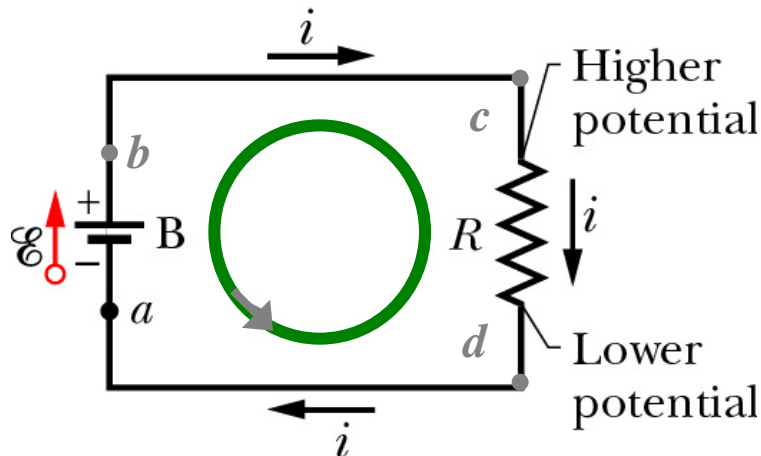

- Traverse counterclockwise from a:

$$\Delta V_{da} = 0$$

$$\Delta V_{cd} = V_c - V_d = +iR$$

$$\Delta V_{bc} = 0$$

$$\Delta V_{ab} = V_a - V_b = -\varepsilon$$

$$\sum_{\text{closed loop}} \Delta V = 0 = 0 + iR + 0 - \varepsilon$$

$$\begin{aligned} iR - \varepsilon &= 0 \\ i &= \frac{\varepsilon}{R} \end{aligned}$$

Equivalent resistance for resistors in series

Junction Rule: The current through all of the resistances in series (a single branch) is identical:

$$\mathbf{i = i_1 = i_2 = i_3}$$

Loop Rule: The sum of the potential differences around a closed loop equals zero:

$$\varepsilon - iR_1 - iR_2 - iR_3 = 0 \quad \Rightarrow \quad \mathbf{i = \frac{\varepsilon}{R_1 + R_2 + R_3}}$$

The equivalent circuit replaces the series resistors with a single equivalent resistance:

same \mathcal{E} , same i as above



$$\varepsilon - iR_{\text{eq}} = 0 \quad \Rightarrow \quad \mathbf{i = \frac{\varepsilon}{R_{\text{eq}}}}$$

The equivalent resistance for a series combination is the sum of the individual resistances and is always greater than any one of them.

$$\mathbf{R_{\text{eq}} = R_1 + R_2 + R_3}$$

$$\mathbf{R_{\text{eq}} = \sum_{i=1}^n R_i}$$

inverse of series capacitance rule

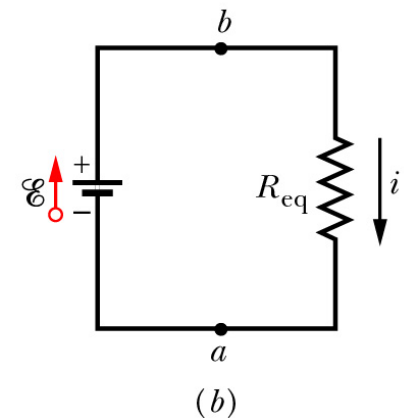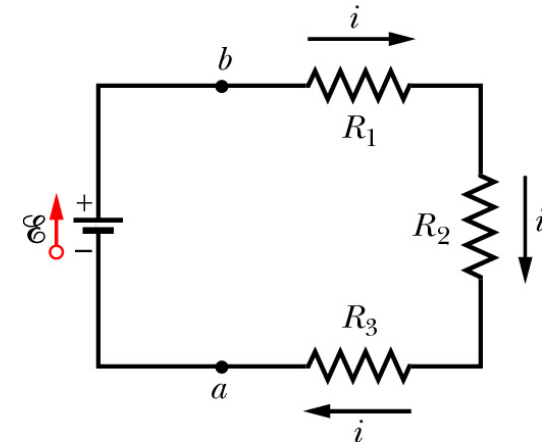

Equivalent resistance for resistors in parallel

Loop Rule: The potential differences across each of the parallel branches are the same.

$$\begin{aligned} \mathcal{E} - i_1 R_1 &= 0 & \mathcal{E} - i_2 R_2 &= 0 & \mathcal{E} - i_3 R_3 &= 0 \\ i_1 &= \frac{\mathcal{E}}{R_1}, & i_2 &= \frac{\mathcal{E}}{R_2}, & i_3 &= \frac{\mathcal{E}}{R_3} \end{aligned}$$

i not in equations

Junction Rule: The sum of the currents flowing in equals the sum of the currents flowing out. Combine equations for all the junctions at “a” & “b”.

$$i = i_1 + i_2 + i_3 = \mathcal{E} \left(\frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3} \right)$$

The equivalent circuit replaces the series resistors with a single equivalent resistance:

same \mathcal{E} , same *i* as above



$$\mathcal{E} - i R_{\text{eq}} = 0 \quad \Rightarrow \quad i = \frac{\mathcal{E}}{R_{\text{eq}}}$$

The reciprocal of the equivalent resistance for a parallel combination is the sum of the individual reciprocal resistances and is always smaller than any one of them.

$$\frac{1}{R_{\text{eq}}} = \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3}$$

$$\frac{1}{R_{\text{eq}}} = \sum_{i=1}^n \frac{1}{R_i}$$
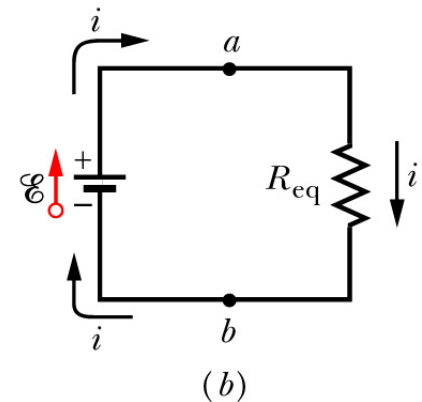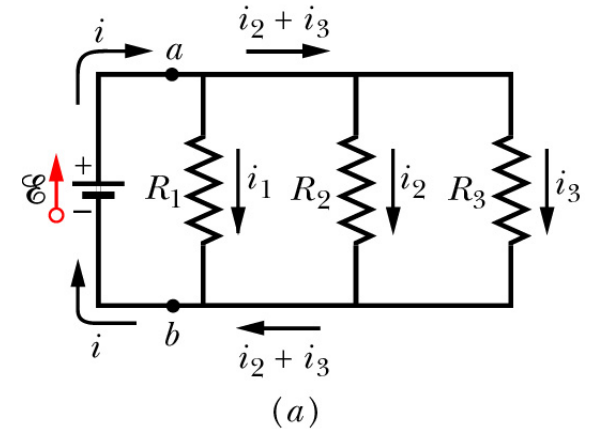
$$R_{\text{eq}} = \frac{R_1 R_2}{R_1 + R_2}$$




inverse of parallel capacitance rule

Resistors in series and parallel

7-7: Four identical resistors are connected as shown in the figure. Find the equivalent resistance between points *a* and *c*.

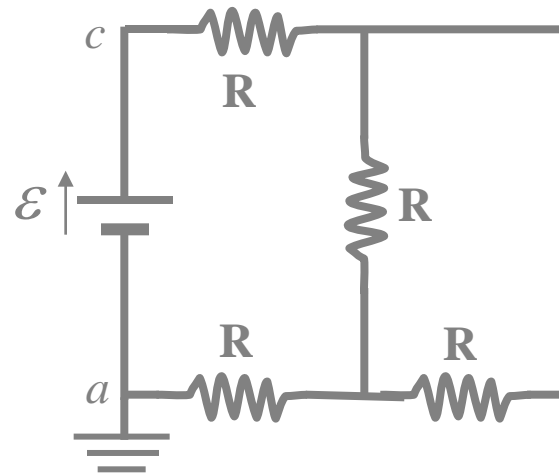- A. 4 R.
- B. 3 R.
- C. 2.5 R.
- D. 0.4 R.
- E. Cannot determine from information given.




$$\frac{1}{R_{\text{eq}}} = \sum_{i=1}^n \frac{1}{R_i}$$

$$R_{\text{eq}} = \sum_{i=1}^n R_i$$

Capacitors in series and parallel

7-8: Four identical capacitors are connected as shown in figure. Find the equivalent capacitance between points *a* and *c*.

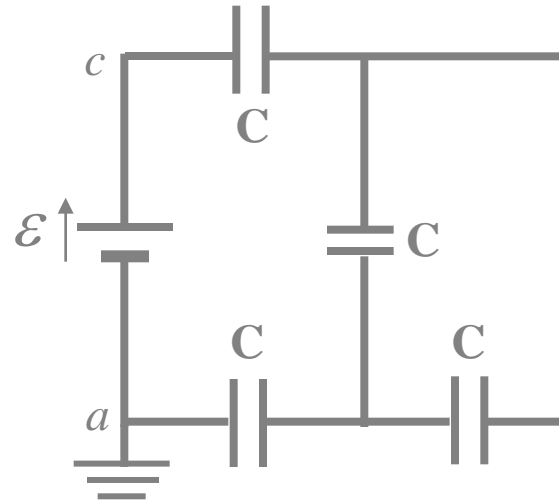- A. 4 C.
- B. 3 C.
- C. 2.5 C.
- D. 0.4 C.
- E. Cannot determine from information given.




$$\frac{1}{C_{\text{eq}}} = \sum_{i=1}^n \frac{1}{C_i}$$

$$C_{\text{eq}} = \sum_{i=1}^n C_i$$

EXAMPLE:

Find i , V_1 , V_2 , V_3 , P_1 , P_2 , P_3

7

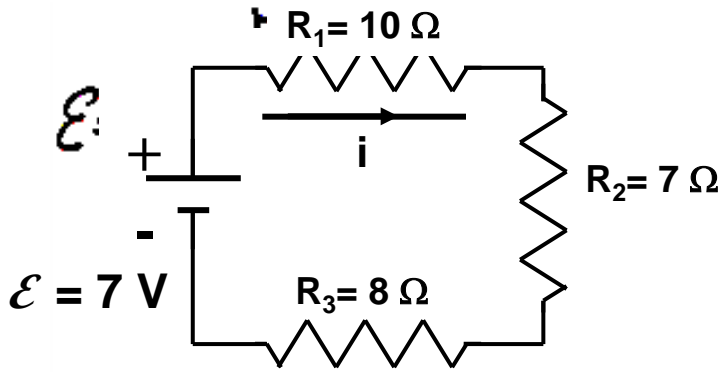

$$i = \frac{\mathcal{E}}{R_{eq}} = \frac{7}{10+7+8} = \frac{7}{25} = 0.28 \text{ A}$$

$$V_1 = iR_1 = 0.28 \times 10 = 2.80 \text{ V}$$

$$V_2 = iR_2 = 0.28 \times 7 = 1.96 \text{ V}$$

$$V_3 = iR_3 = 0.28 \times 8 = 2.24 \text{ V}$$

$$\underline{V} = \underline{7 \text{ V}}$$

$$P_1 = i^2 R_1 = (0.28)^2 \times 10 = 0.78 \text{ W} = iV = (0.28) \times 2.8$$


$$P_2 = i^2 R_2 = (0.28)^2 \times 7 = 0.55 \text{ W}$$

$$P_3 = i^2 R_3 = (0.28)^2 \times 8 = 0.627 \text{ W}$$

$$\underline{P} = 1.96 \text{ W} = \underline{iV} = \underline{1.96 \text{ W} \leftarrow \text{SUM}}$$

EXAMPLE: $R_1 = 4\Omega$, $R_2 = 11\Omega$.

Find currents and voltage drops

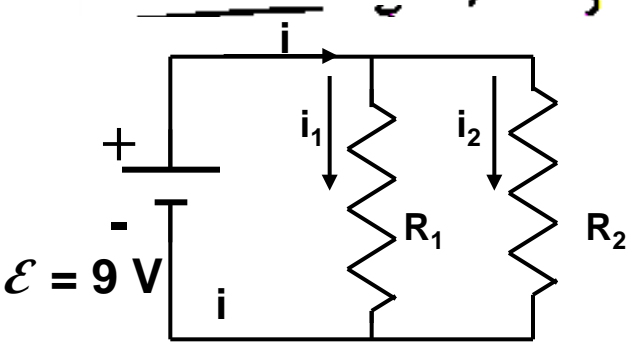

Loop Rule: $\mathcal{E} - i_1 R_1 = 0$ $\mathcal{E} - i_2 R_2 = 0$

$$\Rightarrow i_1 R_1 = i_2 R_2 = 9 \text{ volts}$$

Current Rule: $i_1 = \frac{9}{4} = 2.25 \text{ A}$ $i_2 = \frac{9}{11} \text{ A}$


OR: Final $R_{eq} = \frac{4 \times 11}{4+11} = 2.93 \Omega$

$$i = \frac{\mathcal{E}}{R_{eq}} = 3.07 \text{ A}$$

$$R_{eq} = \frac{R_1 R_2}{R_1 + R_2}$$

$$P_2 = i_2^2 R_2 = 7.36 \text{ W}$$

EXAMPLE: MULTIPLE BATTERIES
SINGLE LOOP

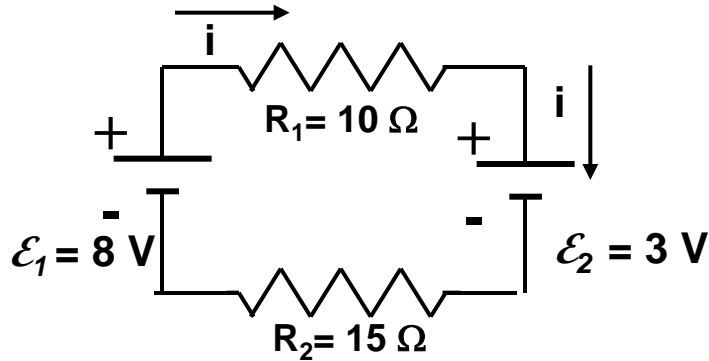

Final $i, P_{\epsilon_1}, P_{\epsilon_2}, P_{R_1}, P_{R_2}$


LOOP RULE:

$$\epsilon_1 - iR_1 - \epsilon_2 - iR_2 = 0$$

$$\epsilon_1 - \epsilon_2 = i(R_1 + R_2)$$

$$i = \frac{\epsilon_1 - \epsilon_2}{(R_1 + R_2)} = \frac{8 - 3}{10 + 15} = 0.2 \text{ A}$$

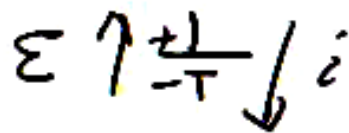A battery (EMF) absorbs power (charges up) when I is opposite to E



$$P_{\text{emf}} = \pm \epsilon i = \vec{\epsilon} \cdot \vec{i}$$

$$P_{\epsilon_1} = \epsilon_1 i = 8 \times 0.2 = 1.6 \text{ W} \text{ PROVIDED TO CIRCUIT}$$

$$P_{\epsilon_2} = \epsilon_2 i = -3 \times 0.2 = -0.6 \text{ W absorbed}$$

$$P_{R_1} = i^2 R_1 = (0.2)^2 \times 10 = 0.4 \text{ W dissipated}$$

$$P_{R_2} = -i^2 R_2 = -(0.2)^2 \times 15 = -0.6 \text{ W "}$$

-1.6 Watts

$$P_{\epsilon_1} = P_{\epsilon_2} + P_{R_1} + P_{R_2}$$

EXAMPLE: Find the average current density J in a copper wire whose diameter is 1 mm carrying current of $i = 1$ ma.

$$J = \frac{i}{A} = \frac{10^{-3} \text{ amps}}{\pi \times (.5 \times 10^{-3} \text{ m})^2} = 1273 \text{ amps/m}^2$$

Suppose diameter is 2 mm instead. Find J' :

$$J' = \frac{i}{A'} = \frac{J}{4} = 318 \text{ amps/m}^2 \quad \text{Current } i \text{ is unchanged}$$

Calculate the drift velocity for the 1 mm wire as above?

$$J = en_{\text{Cu}}v_d \quad \text{where} \quad n_{\text{Cu}} = \# \text{ conduction electrons/m}^3 \approx 8.49 \times 10^{28}$$

$$v_d = \frac{J}{en_{\text{Cu}}} = \frac{1273}{1.6 \times 10^{-19} \times 8.49 \times 10^{28}} = 9.37 \times 10^{-8} \text{ m/s} \quad \text{About 3 m/year !}$$

So why do electrical signals on wires seem to travel at the speed of light (300,000 km/s)?

Calculating n for copper: One conduction electron per atom

$$\begin{aligned} n_{\text{Cu}} &= 1 \text{ electron/atom} \times \frac{8.96 \text{ gm/cm}^3}{63.5 \text{ gm/mole}} \times 6.02 \times 10^{23} \text{ atoms/mole} \times 10^6 \text{ cm}^3/\text{m}^3 \\ &= 8.49 \times 10^{28} \text{ electrons/m}^3 \end{aligned}$$